

UNIVERSITY OF RUHUNA - FACULTY OF TECHNOLOGY
BACHELOR OF ENGINEERING TECHNOLOGY
Level 2 (Semester 1) Examination, October 2018

COURSE UNIT: ENT2113 ANALOGUE ELECTRONIC SYSTEM
Time Allowed: 3 hours

Note: Answer all four (05) questions
All symbols have their usual meaning

Question 01

- (a) State the Thevenin's theorem and Norton's theorem.
- (b)
- The Thevenin equivalent circuit of a network consists of a voltage of 9 V in series with an impedance of 2Ω . Find the Norton equivalent of circuit.
 - The Norton equivalent circuit of a network consists of a 12A in parallel with an impedance of 3Ω . Find the Thevenin equivalent of circuit.
- (c) Figure Q01(c) represents an active network consisting of one voltage source, one current source and four linear resistors. Find the,
- Thevenin equivalent circuit,
 - Norton equivalent circuit, at the terminals A and B.

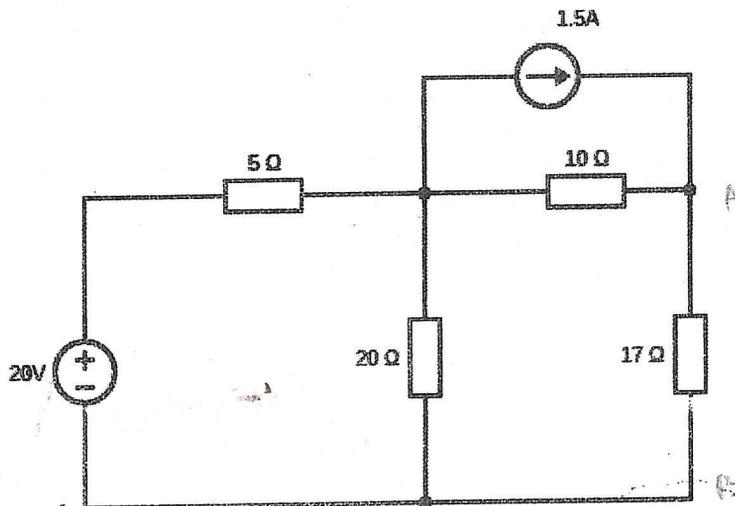


Figure Q01(c)

- (d) Figure Q01(d) shows a Wheatstone bridge, R_1 is a fixed $1k\Omega$ resistor, R_3 can be adjusted in 1Ω steps from 0 to 1100Ω , and R_2 can be selected to be $1k\Omega$, $10k\Omega$, $100k\Omega$ or $1M\Omega$
- Suppose that the bridge is balanced with $R_3=732\Omega$ and $R_2=10k\Omega$. What is the value of R_x ?
 - What is the largest value of R_x which the bridge can be balanced?
 - Suppose that $R_2=1M\Omega$. What is the increment between values of R_x for which the bridge can be precisely balanced?

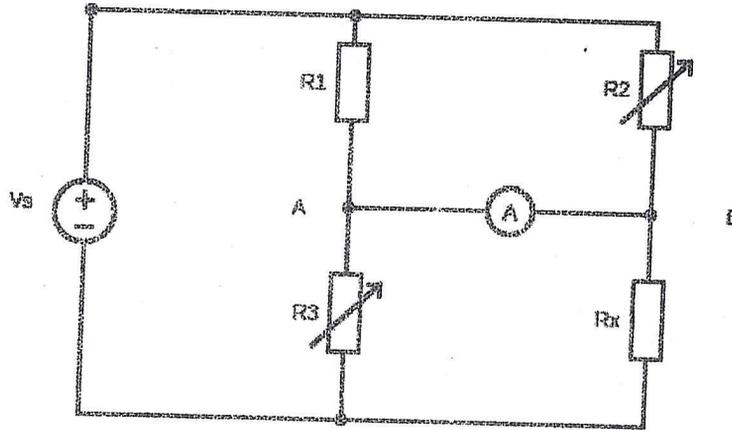


Figure Q01(d)

Question 02

- Draw the circuit symbol and V-I characteristics of a diode.
- What are the half wave and full wave rectification methods, explain it using circuit diagrams.
- Draw the circuit symbol and V-I characteristics of a typical zener diode.
- The load resistance R_L in the voltage regular circuit of Figure Q02(d) is fixed at $10k\Omega$. But the input supply voltage V_1 varies from $80V$ to $120V$.
 - Does zener remain "on" even when the input supply voltage reduces to $80V$?
 - Calculate the maximum value of zener diode current.
 - Calculate the minimum value of zener diode current.

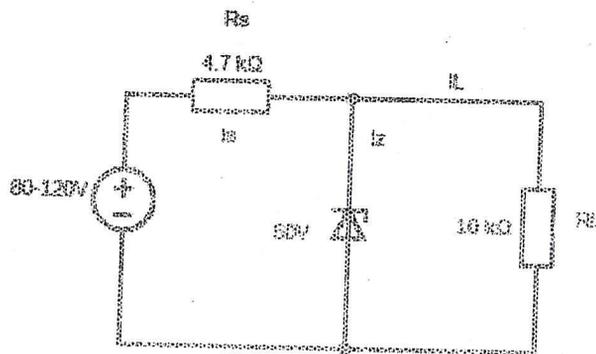


Figure Q02(d)

Question 03

- Name the three Bipolar Junction Transistor(BJT) configurations used in the circuit, and draw circuit diagrams to show each of them using a npn transistor.
- Draw the input and output characteristics of a BJT for Common Emmitter(CE) configuration.
- List three applications of a transistor and briefly explain each of them.
- Consider the common emitter transistor amplifier as shown in figure Q03 (d)
 - Using Thevenin's equivalent circuit, calculate the quiescent voltage and current.
 - Is this amplifier non-inverting or inverting?

Where: $V_{cc}=12V$, $V_{BE}=0.6V$, $R_1=15k\Omega$, $R_2=2.7k\Omega$, $R_C=1k\Omega$, $R_E=220\Omega$, $\beta=100$

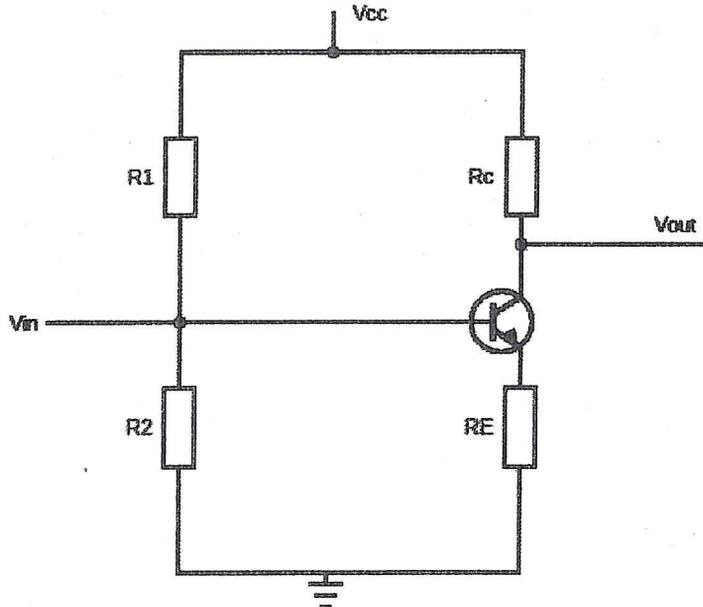


figure Q03 (d)

Question 04

- We use semiconductors to build Field Effect Transistor (FET). Show how those different types of Semiconductors are connected to form FET. Give the circuit symbol of different types of the FET.
- Show the different regions of operation of a FET on its Drain characteristics.
- A certain JFET indicate that $I_{DSS}=3.0mA$, $V_{GS(off)}=(-6V)$ maximum, and $g_{fs(max)}=500\mu S$. Using these values, determine the forward trans conductance for $V_{GS}(-4V)$, and find I_D at this point.

- d) In a self-bias N-channel JFET shown in figure Q04 (d) the operating point is to be set at $I_d = 1.5\text{mA}$ and $V_{ds} = 10\text{V}$. The JFET parameters are $I_{DSS} = 5\text{mA}$ and $V_P = (-2\text{V})$. Find the values of R_S and R_G (Given that $V_{dd} = 20\text{V}$.)


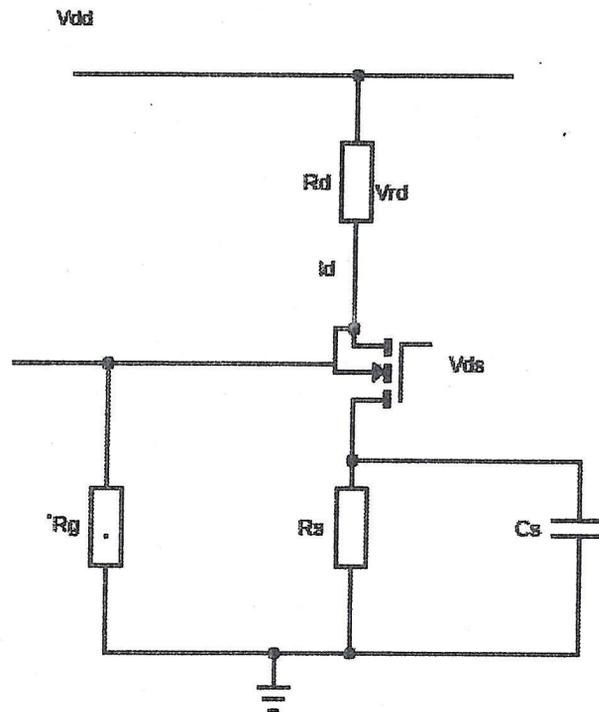


figure Q04 (d)

Question 05

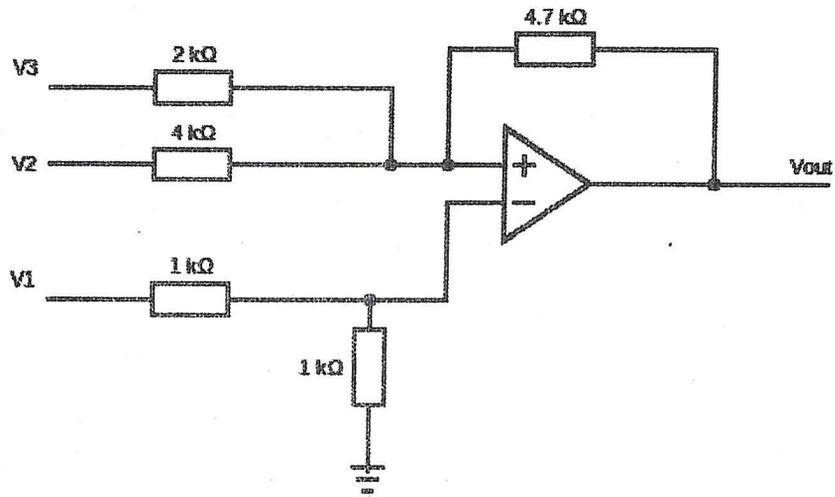- (a) List four characteristics of an ideal operational amplifier (Op-Amp). Compare the ideal values with its typical values.
- (b)
 - I. What are the benefits of negative feedback in an O-Amp circuit?
 - II. Why is it necessary to reduce the gain of an Op-Amp from its open loop gain?
 - III. What do you mean by the term "Virtual ground"?
 - IV. Derive an equation for the closed loop voltage gain for a non-inverting amplifier.
 - V. What is a voltage follower? Explain it using a circuit diagram and find the voltage gain of it?
- (c) Describe the three basic filters and respond characteristic.
- (d) Determine an expression for the output voltage V_{out} in the circuit shown in figure Q05(c). Assume that the operational amplifier is ideal. (If $V_2 = 3\text{V}$ and $V_3 = 2\text{V}$, then find the value of V_1 to get $V_{out} = 0\text{V}$.)



figureQ05(c)