

University of Ruhuna - Faculty of Technology
Bachelor of Engineering Technology Honours Degree
Level 3 (Semester I) Examination, June 2023
Academic year 2021/2022

Course Unit: ENT 3142 – Circuit Analysis and Fault Diagnosis (Written)

Duration: 2 hours

- This paper contains **four (04)** questions on **three (03)** pages.
- Answer all the questions.
- Each question carries equal marks.
- This is a **closed book** examination.

- If you have any problem with the interpretation of a wording of a question you may use your own interpretation clearly mentioning it.
- You may make any suitable assumptions and approximations in your calculations, clearly stating and justifying them where necessary.

Q1. Consider the two-port network shown in Figure Q1a.

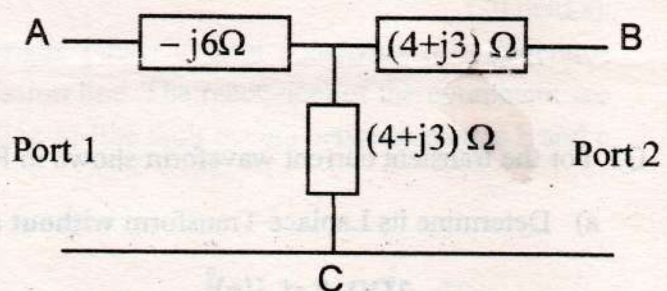


Figure Q1a

- a)
- i. Obtain the **Y-parameter matrix**. (20 marks)
 - ii. Hence, find its **Z-parameter matrix**. (10 marks)

b) Answer the following questions for the circuit shown in Figure Q1b.

- i. Redraw the circuit replacing the voltage source by an **equivalent current source**. (10 marks)
- ii. By suitably numbering the nodes, determine the **node branch incidence matrix**. (20 marks)
- iii. Using the result in part ii) or from other method, determine the **nodal admittance matrix**. (20 marks)
- iv. Using nodal analysis, determine the **branch currents** in all the branches of the original circuit. (20 marks)

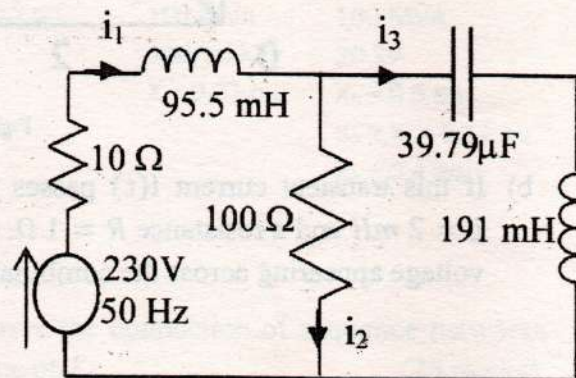


Figure Q1b

Q2. The following Figure Q2a shows the current $i(t)$ passing through a certain device.

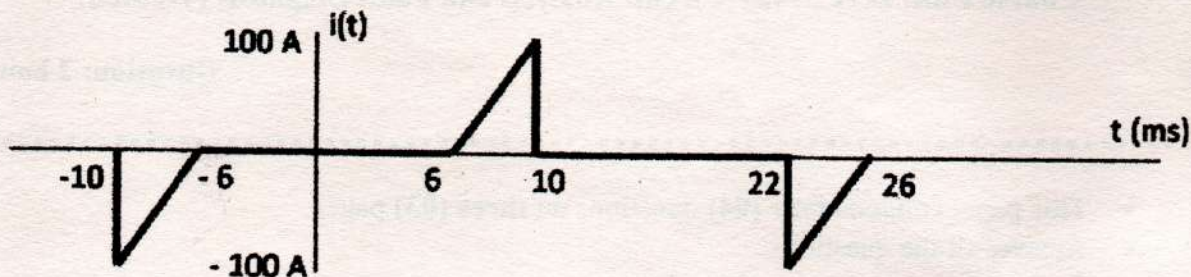


Figure Q2a

- State whether the waveform shows any **symmetrical properties** along with a **mean value**. (15 marks)
- State the significance of these properties in determining the Fourier series. (30 marks)
- What is the **period** and the fundamental **angular frequency** of the waveform? (15 marks)
- Determine the **Fourier series** of this current $i(t)$ to three significant terms. (40 marks)

Q3. For the transient current waveform shown in Figure Q3a,

- Determine its Laplace Transform **without using first principles**. (30 marks)

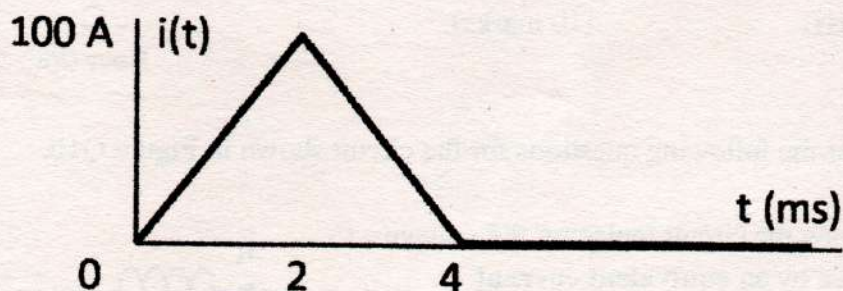


Figure Q3a

- If this transient current $i(t)$ passes through a series combination of an inductance $L = 2 \text{ mH}$ and a resistance $R = 1 \Omega$, determine an expression for the transform of the voltage appearing across the combination. (30 marks)
- Figure Q3b shows a circuit in which the capacitor C is charged to a voltage of $V_0 = 40 \text{ V}$ when the switch S is closed at $t = 0$. If $E_m = 100 \text{ V}$, $\omega = 250 \text{ rad/s}$, $L = 50 \text{ mH}$, $r = 10 \Omega$, $R = 100 \Omega$, $C = 40 \mu\text{F}$, draw the equivalent circuit in the Laplace domain, indicating all significant values. (40 marks)

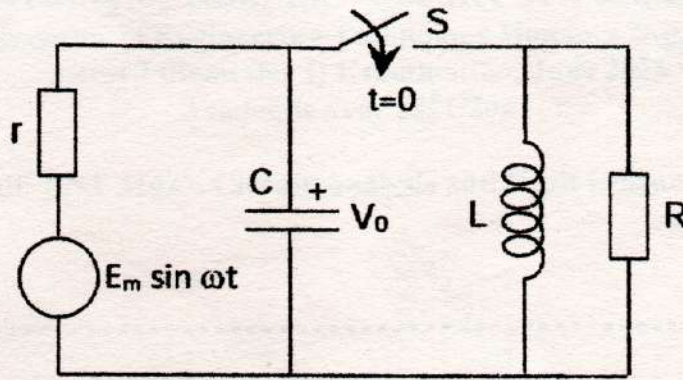


Figure Q3b

Q4.

- State the basic two (02) types of **power system faults**. (10 marks)
- Show that when the **three unbalanced phasors** a, b and c are represented by positive, negative and zero sequences, the unbalanced phasors and the **sequence networks** are related through the matrix,

$$\begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix}$$

where $\alpha = 1 \angle 120^\circ$.

(20 marks)

- The following Figure Q4a shows a simple power system consisting of a generator feeding a motor load through a transmission line. The reactances of the equipment are mentioned underneath them. A bolted line-to-line fault occurs between phases b and c at the location shown.

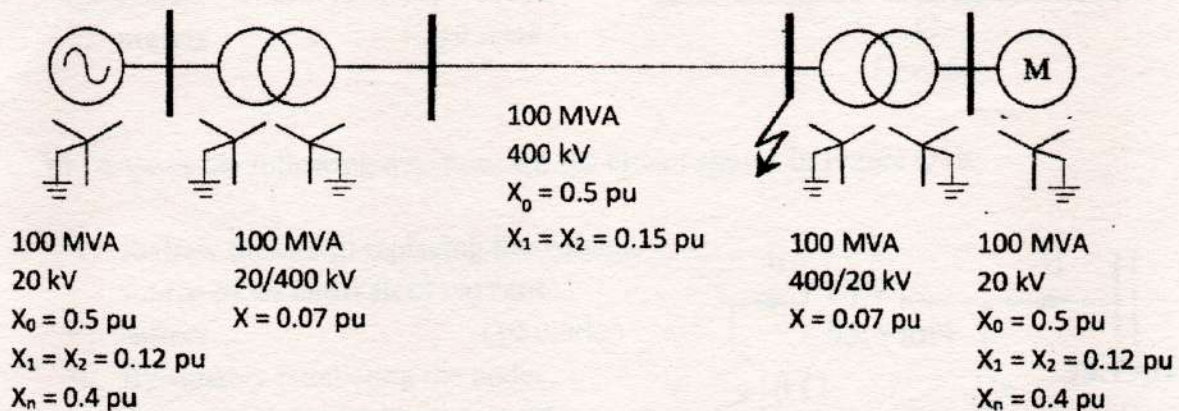


Figure Q4a

- Using symmetrical component analysis, derive the connection of sequence networks for a **line-to-line fault** with a fault impedance of Z_f . (25 marks)
- For a bolted line-to-line fault at the shown location, obtain the **positive, negative and zero** sequence networks considering $S_{base} = 100$ MVA. (30 marks)
- Determine the magnitudes of currents in each phase during the fault. (15 marks)

----- End of the paper -----