



UNIVERSITY OF RUHUNA

Faculty of Engineering

End-Semester 6 Examination in Engineering: November 2022

Module Number: EE6205

Module Name: Hardware Description Language

[Three Hours]

[Answer all questions, each question carries 10 marks]

- Q1 a) (i) Describe four (04) advantages of using HDL for electronic design over schematic diagrams. [2.0 Marks]
- (ii) Differentiate programming language for CPUs and Hardware Description Language. [1.0 Mark]
- b) (i) State two (02) main paths in VLSI design. [1.0 Mark]
- (ii) Compare ASIC and FPGA in terms of their pros and cons. [2.0 Marks]
- (iii) Explain the role of Test Bench in VLSI design verification. [1.0 Mark]
- c) As an electronic design engineer, you are asked to design a 4-way traffic light controller.
- (i) Suggest three (03) design approaches to design the circuit. [1.0 Mark]
- (ii) Justify the use of HDL to design the above-mentioned system. [2.0 Marks]
- Q2 a) Name and describe two (02) main components of a VHDL design. [1.0 Mark]
- b) Why is it a good approach to draw a black-box diagram when using VHDL to model digital circuits? [1.0 Mark]
- c) Write the VHDL entity declaration that describes the black-box diagram shown in Figure Q2 c). [3.0 Marks]

 


Figure Q2 c)

- d) Name and explain the three (03) main modeling styles that can be used to describe the internal implementation of the associated entity. [3.0 Marks]
- e) Write a VHDL code to implement the following Boolean function using concurrent signal assignment.

$$F(A, B) = \bar{A}B + A + A\bar{B}$$

[2.0 Marks]

- Q3 a) Explain the difference between types 'wire' and 'reg' in Verilog. [1.0 Mark]

- b) (i) Write a Verilog module to implement a 1-bit full adder and name it as **full_adder**. [2.0 marks]

- (ii) Design a 4-bit full adder using Verilog incorporating the **full_adder** module in Q3 b (i). [3.0 marks]

- (iii) Write two (02) Test Benches to test the 1-bit full adder and 4-bit full adder. [4.0 Marks]

- Q4 Figure Q4 shows a Serial-in Serial-out (SISO) Shift register.

- a) Implement the SISO Shift register shown in Figure Q4 using VHDL. [4.0 Marks]

- b) Explain the difference between blocking and non-blocking statements in Verilog. [2.0 Marks]

- c) Implement the SISO Shift register shown in Figure Q4 using Verilog. [4.0 Marks]

 


Figure Q4

- Q5 a) Explain the role of LUTs and D Flip-flops in FPGAs. [2.0 Mark]

- b) State two (02) main constraint files required in FPGA. [1.0 Mark]

- c) Name and explain the standard way to communicate between 2 different modules in FPGA? [1.0 Mark]

- d) State two (02) main timing failures that happen in FPGA designs and explain how those timing failures are corrected. [3.0 Marks]

- e) Explain main steps of designing a digital system using FPGA. [3.0 Marks]