



# UNIVERSITY OF RUHUNA

## Faculty of Engineering

End-Semester 3 Examination in Engineering: July 2022

Module Number: EE3301

Module Name: Analog Electronics

[Three Hours]

[Answer all questions, each question carries 10 marks]

- Q1 a) Figure Q1.1 shows a fixed biased N-channel JFET. Here,  $V_{DD} = 16V$ ,  $V_{GS} = -1.5V$  and  $R_D = 2k\Omega$ .
- Find the Q point ( $I_D$ ,  $V_{DS}$ ) of the circuit  $I_{DSS} = 10mA$  and  $V_P = -4V$ .
  - Find the Q point ( $I_D$ ,  $V_{DS}$ ) of the circuit if  $I_{DSS}$  and  $V_P$  are changed to  $12mA$  and  $-4.2V$ .

 


Figure Q1.1

[4.0 Marks]

- b) Figure Q1.2 shows a self-biased N-channel JFET. Here,  $V_{DD} = 16V$ ,  $R_S = 375\Omega$  and  $R_D = 2k\Omega$ .
- Find the Q point ( $I_D$ ,  $V_{DS}$ ) of the circuit, when  $I_{DSS} = 10mA$  and  $V_P = -4V$ .
  - Find the Q point ( $I_D$ ,  $V_{DS}$ ) of the circuit, if  $I_{DSS}$  and  $V_P$  are changed to  $12mA$  and  $-4.2V$ .

 


Figure Q1.2

[4.0 Marks]

- c) Explain the advantage of self-biasing over fixed biasing based on the answers obtained for Q1. a) and Q1. b).

[2.0 Marks]

- Q2 a) Briefly compare CMOS and Bipolar technologies [2.0 Marks]
- b) Briefly explain the importance of current mirrors in analog IC design. [2.0 Marks]
- c) Figure Q2 shows a current mirroring circuit for three transistors, namely, Q1, Q2, and Q3.
- Approximate the Q points ( $I_C, V_{CE}$ ) of Q1, Q2, and Q3.
  - Find the exact (rounded to 2 decimal places) Q points ( $I_C, V_{CE}$ ) of Q1, Q2, and Q3. Note that  $\beta = 150$ .

 


Figure Q2

- Q3 a) Briefly explain the DC offset of an operational amplifier. [6.0 Marks]
- b) Figure Q3 shows an integrating amplifier. [2.0 Marks]
- Derive an expression for the output  $v_o$  of the integrating circuit in time( $t$ ) domain assuming the ideal conditions of the operational amplifier.
  - Derive an expression for the output  $v_o$  of the integrating circuit in time( $t$ ) domain considering the DC offset as  $v_{os}$ , where  $v_s = 0$ .
  - Briefly explain why the circuit shown in Figure Q3 is incapable of delivering the expected output with the DC off-set.
  - Propose a modified circuit for the integrating amplifier that will compensate the DC offset's effect.

 


Figure Q3

[8.0 marks]

Q4 a) Answer the following questions based on Figure Q4.1.

- i. Derive an expression for the output  $v_o$  of the amplifier circuit.
- ii. Identify the mathematical operation performed by the circuit.

 


Figure Q4.1

[4.0 Marks]

- b) Figure Q4.2 shows a mathematical model of a neuron, the basic building block of artificial neural networks. Analog circuits based on op-amps can be used to implement mathematical functions. Propose a circuit to compute the output of the mathematical model of a neuron where the neuron receives 3 inputs ( $n = 3$ ) and the  $\phi$ , or the activation function is ReLU (Rectified Linear Unit).

 


Figure Q4.2

[6.0 Marks]

Q5 a) Explain the difference between passive and active analog filters.

[1.0 Mark]

b) Explain each of the following in relation to analog filters.

i) Function of a filter.

ii) Bode plot.

[1.0 Mark]

c) Draw a circuit of a simple high pass filter and explain how the output is being controlled by the components in the circuit

[3.0 Marks]

d) Design a second-order VCVS low-pass Butterworth filter with cut-off frequency 2.5 kHz. The gain in the pass band should be 2. The VCVS design or Sallen-Key circuit is given in Figure Q5.1. You may use any of the charts given in Figure Q5.2.

You may use  $C = 0.05 \mu\text{F}$  (If this result in impractical values revise the choice).

[5.0 Marks]

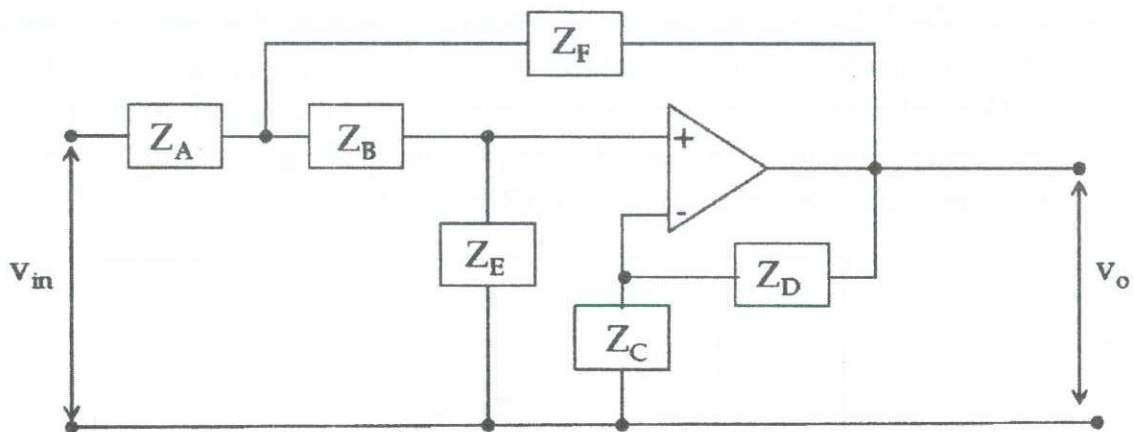


Figure Q5.1



**Table 14-1**  
VCVS Filter Components

	$Z_A$	$Z_B$	$Z_C$	$Z_D$	$Z_E$	$Z_F$
Low-Pass Filter	$R_1$	$R_2$	$R_3$	$R_4$	$C_1$	$C$
High-Pass Filter	$C$	$C$	$R_3$	$R_4$	$R_2$	$R_1$

**Table 14-2**  
Second-Order Low-Pass Butterworth VCVS Filter Designs

Gain	Circuit Element Values <sup>a</sup>					
	1	2	4	6	8	10
$R_1$	1.422	1.126	0.824	0.617	0.521	0.462
$R_2$	5.399	2.250	1.537	2.051	2.429	2.742
$R_3$	Open	6.752	3.148	3.203	3.372	3.560
$R_4$	0	6.752	9.444	16.012	23.602	32.038
$C_1$	0.33C	C	2C	2C	2C	2C

<sup>a</sup> Resistances in kilohms for a K parameter of 1.

**Table 14-3**  
Second-Order Low-Pass Chebyshev VCVS Filter Designs (2 dB)

Gain	Circuit Element Values <sup>a</sup>					
	1	2	4	6	8	10
$R_1$	2.328	1.980	1.141	0.786	0.644	0.561
$R_2$	13.220	1.555	1.348	1.957	2.388	2.742
$R_3$	Open	7.069	3.320	3.292	3.466	3.670
$R_4$	0	7.069	9.959	16.460	24.261	33.031
$C_1$	0.1C	C	2C	2C	2C	2C

<sup>a</sup> Resistances in kilohms for a K parameter of 1.

**Table 14-4**  
Second-Order High-Pass Chebyshev VCVS Filter Designs (2 dB)

Gain	Circuit Element Values <sup>a</sup>					
	1	2	4	6	8	10
$R_1$	0.640	1.390	2.117	2.625	3.040	3.399
$R_2$	3.259	1.500	0.985	0.794	0.686	0.613
$R_3$	Open	3.000	1.313	0.953	0.784	0.681
$R_4$	0	3.000	3.939	4.765	5.486	6.133

<sup>a</sup> Resistances in kilohms for a K parameter of 1.

Source: Reprinted from *Rapid Practical Designs of Active Filters*, D. Johnson and J. Hilburn. Copyright © 1975, John Wiley and Sons, Inc., by permission of John Wiley and Sons, Inc.

Figure Q5.2