



UNIVERSITY OF RUHUNA

Faculty of Engineering

Mid-Semester 3 Examination in Engineering: June 2014

Module Number: EE3304

Module Name: Electrical Machines

[Two Hours]

[Answer all questions, each question carries 5 marks]

Q1 a) Briefly explain the four basic principles which describe the fundamentals in electrical machines' operation. [1.0 Mark]

b) What are the types of losses take place in a ferromagnetic core? What precautionary actions can be taken to minimize the above losses? [1.0 Mark]

c) Figure Q1 shows a static magnetic field rotating at an angular speed of ω , in the center of a rectangular shape ($2r$ width, l length) stationary coil.

i) Show that the induced voltage of the coil is given by,

$$e_{ind} = N_c(2Brl)\omega \sin \omega t$$

where,

N_c - Number of turns in the coil

t - Time

B - Flux density

ii) The flux density and the rate of rotation of the rotating magnetic field mentioned in part c) (i), is 0.3 Wb/m^2 and 1200 rpm , respectively. The coil length is 0.4 m and the width is 0.5 m . If the coil consists of 15 turns, express the induced voltage as a function of time and hence calculate the rms voltage of the coil. [3.0 Marks]

Q2. a) The transformer model parameters can be adequately approximated using the open circuit and the short circuit tests for a given transformer. Briefly explain the method of performing these tests. [1.5 Marks]

b) A 2 kVA , $230/115 \text{ V}$ transformer has been tested to determine its equivalent circuit. The results of the tests are shown below

Open Circuit Test

$I_{oc} = 0.45 \text{ A}$

$P_{oc} = 30 \text{ W}$

Short Circuit Test

$V_{sc} = 19.1 \text{ V}$

$P_{sc} = 42.3 \text{ W}$

All data given were taken from the primary side of the transformer.

i) Find the equivalent circuit of this transformer referred to the low-voltage side.

ii) Determine the voltage regulation and the efficiency of the transformer at rated conditions and 0.8 power factor lagging. [3.5 Marks]

Q3. a) What are the types of losses take place in an induction motor? Draw the power flow diagram indicating how the power flows through an induction motor. [1.0 Mark]

b) A 208 V, two-pole, 60 Hz Y-connected wound-rotor induction motor is rated at 15 hp. The motor operates a load with the speed of 3420 rpm. The rotational and the core losses of the machine are 250 W and 180 W, respectively Its equivalent circuit parameters are

$$R_1 = 0.20 \Omega \quad R_2' = 0.12 \Omega \quad X_m = 15 \Omega$$

$$X_1 = 0.41 \Omega \quad X_2' = 0.41 \Omega$$

Note that all the notations have their usual meanings.

- Find the air gap power (P_{AG}).
- Calculate the induced torque (τ_{ind}) and the load torque (τ_{load}).
- Calculate the overall efficiency of the machine.

[4.0 Marks]

Q4. a) Briefly explain the rotor resistance starting method for a wound rotor induction motor. [1.0 Mark]

[1.0 Mark]

b) Consider the induction motor given in Q3 part b)

- Calculate the speed at which the induction motor gives its maximum torque.
- How much additional resistance would be necessary to add to the rotor circuit to make the maximum torque occur at starting condition?

[4.0 Marks]

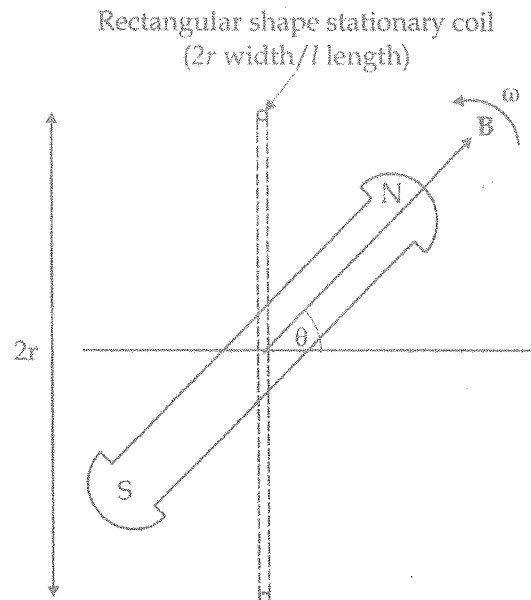


Figure Q1