



# UNIVERSITY OF RUHUNA

## Faculty of Engineering

End-Semester 3 Examination in Engineering: February 2023

Module Number: EE3301

Module Name: Analog Electronics (C-18)

[Three Hours]

[Answer all questions, each question carries 10 marks]

[Attach the question paper to your answer script. Failing which, you will get zero for Q3]

- Q1 a) State three FET biasing mechanisms. [2 Marks]
- b) Draw the voltage divider biasing circuit for a N- Channel JFET. [2 Marks]
- c) Figure Q1 shows a biased stabilized JFET amplifier with  $g_m = 2\text{mS}$ ,  $r_{ds} = 30\text{ k}\Omega$ ,  $R_S = 3\text{ k}\Omega$ ,  $R_D = R_L = 2\text{ k}\Omega$ ,  $R_1 = 200\text{ k}\Omega$ ,  $R_2 = 800\text{ k}\Omega$  and  $r_i = 5\text{ k}\Omega$ . The values of  $C_C$  and  $C_S$  are large and the amplifier is biased in the pinch off region.
- Draw the small signal equivalent circuit.
  - Find  $Z_{in}$
  - Find  $A_v = v_L/v_i$
  - Find  $A_i = i_L/i_i$

 


Figure Q1

[5 Marks]

- d) What is the purpose of  $C_S$  capacitor in Figure Q1 circuit diagram?

[1 Mark]

Q2 a) Briefly explain the importance of current mirrors in analog IC designs. [1 Mark]

b) Figure Q2 shows a basic current mirror. Prove that the source current  $I$  in the circuit is mirrored to the collector current of transistor T2.

 


Figure Q2

[2 Marks]

c) i) Draw the circuit diagram of an ideal differential amplifier that has a collector resistors  $R_C$ , bias voltage  $+V_{CC}$  and a constant current source  $I$ .

ii) Perform DC analysis for the circuit to derive expressions for the DC output voltages.

[3 Marks]

d) A BJT differential amplifier is biased from a 1 mA constant current source and includes a  $200\ \Omega$  resistor in each emitter. The collectors are connected to  $V_{CC}$  via  $12\ \text{k}\Omega$  resistors. A differential input signal of 0.1 V is applied between the two bases. Find the currents in the emitter  $i_e$  and the voltage  $v_{be}$  for each BJT

[4 Marks]

Q3 Answer Q3 in the space provided and attach the question paper to your answer script.

- a) Complete the circuit shown in Figure Q3a in the space provided, to receive the output  $v_{out} = -(v_1 + v_2 + v_3)$  where  $v_1, v_2, v_3$  are inputs. The feedback resistor value,  $R_f = 10 \text{ k}\Omega$ . Clearly mark the resistors and voltages in the diagram.

 


Figure Q3a

[2 Marks]

- b) For the following questions circle ONE answer that best fits the questions.

[8 Marks]

- i) Find the output  $V_o$  shown in the circuit in Figure Q3b - i. Assume an ideal op-amp.

- A)  $-3.8 \text{ V}$       B)  $-5.7 \text{ V}$       C)  $-0.3428 \text{ V}$       D)  $0.3428 \text{ V}$       E) None of the above

 


Figure Q3b - i

- ii) Find the output voltage  $V_o$  in the circuit shown in Figure Q3b - ii.  
 A) -1 V    B) 6 V    C) -7 V    D) -6 V    E) Insufficient Information

 


Figure Q3b - ii

- iii) For the difference amplifier circuit shown in Figure Q3b - iii, determine the output voltage at terminal A.  
 A) 6.07 V    B) -15.45 V    C) -18.13 V    D) -6.07 V    E) -3.54 V

 


Figure Q3b - iii

- iv) The output of an op-amp increases 8 V in 12  $\mu$ s. The slew rate is \_\_\_\_\_.  
 A) 1.5V/ $\mu$ s    B) 0.6 V/ $\mu$ s    C) 96 V/ $\mu$ s    D) 0.667 V/ $\mu$ s    E) None of these
- v) For an op-amp with negative feedback, the output is \_\_\_\_\_.  
 A) Magnitude is decreased  
 B) Fed back to the inverting input  
 C) Equal to the input  
 D) Increased  
 E) Fed back to the non-inverting input
- vi) Op-amp integrator uses \_\_\_\_\_ as a feedback element.  
 A) Inductor  
 B) A simple wire  
 C) Capacitor  
 D) Resistor  
 E) Any of the above

- vii) Find the input voltage of an ideal op-amp if one of the inputs is 2 V and the output is 12V, with a gain of 3.
- A) - 4 V
  - B) - 2 V
  - C) 8 V
  - D) 4 V
  - E) None of the above
- viii) The common-mode gain of op-amp should be \_\_\_\_\_.
- A) Always unity
  - B) Unpredictable
  - C) Very high
  - D) Very low
  - E) Not enough information
- ix) In differential-mode, \_\_\_\_\_.
- A) The outputs are of different amplitudes
  - B) The outputs are of different polarities
  - C) Opposite polarity signals are applied to the inputs
  - D) The gain is unity
  - E) Only one supply voltage is used
- x) An op-amp can amplify \_\_\_\_\_.
- A) DC signals only
  - B) AC signals only
  - C) Neither AC nor DC signals
  - D) Both AC and DC signals
  - E) Not sufficient information
- xi) A voltage follower \_\_\_\_\_.
- A) Has no feedback resistor
  - B) Has a voltage gain of 1
  - C) Is non-inverting
  - D) Has all of the above A, B and C
  - E) Has none of the above A, B or C
- xii) The ideal op-amp has the following characteristics
- A)  $R_{in} \rightarrow \infty, A_v \rightarrow \infty, R_{out} = \infty$
  - B)  $R_{in} \rightarrow 0, A_v \rightarrow \infty, R_{out} = \infty$
  - C)  $R_{in} \rightarrow \infty, A_v \rightarrow \infty, R_{out} = 0$
  - D)  $R_{in} \rightarrow 0, A_v \rightarrow \infty, R_{out} = 0$
  - E) None of the above
- xiii) A common mode signal is applied to \_\_\_\_\_.
- A) Both inputs
  - B) One of the inputs
  - C) The non-inverting input
  - D) The inverting input
  - E) Top of the tail resistor

xiv) A non-inverting amplifier has  $R_{in} = 1 \text{ k}\Omega$  and  $R_f = 100 \text{ k}\Omega$ . The closed-loop voltage gain is \_\_\_\_\_.

- A) 100      B) 1.01      C) 1000      D) 101      E) 0.01

xv) When a step-input is given to an op-amp integrator, the output will be a \_\_\_\_\_.

- A) Rectangular Wave  
B) Triangular Wave  
C) Ramp  
D) Sinusoidal Wave  
E) Not enough information

xvi) For an op-amp having differential gain  $A_v$  and common mode gain  $A$ , the Common Mode Rejection Ratio (CMRR) is given by \_\_\_\_\_.

- A)  $A_v + 1/A$   
B)  $A/A_v$   
C)  $A_v + A$   
D)  $A_v/A$   
E) None of the above

Q4 a) Predict how the operation of this operational amplifier circuit shown in Figure Q4a will be affected as a result of the following faults. Consider each fault independently (i.e. one at a time, no multiple faults occurring simultaneously).

- i) Resistor  $R_2$  fails open:  
ii) Solder bridge (short) across resistor  $R_2$ :  
iii) Resistor  $R_1$  fails open:  
iv) Solder bridge (short) across resistor  $R_1$ :  
v) Broken wire between  $R_1/R_2$  junction and inverting opamp input:

 


Figure Q4a

[5 Marks]

- b) Figure Q4b shows an op-amp circuit.
- i) Calculate the output voltage  $V_{out}$ .
- ii) Calculate the voltage drops across resistors  $R_1$  and  $R_2$ .
- iii) Calculate the overall voltage gain of this amplifier circuit (given by  $A$ ), both as a ratio and in units of decibels (dB):

 


Figure Q4b

[5 Marks]

- Q5 a) Answer each of the following in relation to analog filters.
- Explain the difference between high pass filter and a notch filter.
  - Explain the difference between passive analog filters and active analog filters, mentioning the components that are used.
  - What does a bode plot indicate?

[5 Marks]

- b) Find the bandwidth of the given filter in Figure Q5 and draw the amplitude response marking the cut off frequencies.  $C = 1.5 \text{ nF}$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ .

 


Figure Q5

[5 Marks]