

University of Ruhuna- Faculty of Technology
Bachelor of Engineering Technology Honours Degree
Level 4 (Semester II) Examination, November/December 2023
Academic year 2021/2022

Course Unit: ENT4223 Power Electronic and Applications

Duration: 3 hours

.....

- The medium of this examination is **English**.
- This is a **closed book** examination.
- This examination consists of **five (05)** questions that are given equal marks.
- Answer **all five (05) questions**.
- This is a **closed book** examination.

01.

a) A single-phase uncontrolled full bridge rectifier is supplied with a sinusoidal AC voltage of 230 V at a frequency of 50 Hz. The load is a resistive load with a resistance of 10 Ω .

- Draw the circuit diagram of the single-phase uncontrolled diode rectifier.
- Draw the output voltage and current waveforms.
- Calculate the followings,
 - Mean value of the output voltage
 - Output power.

(10 marks)

b) A three-phase full bridge uncontrolled diode rectifier is connected a balanced three-phase supply with line-to-line voltage of 400 V (RMS) at a frequency 50 Hz. The load is a resistive load with a resistance of 15 Ω .

- Draw the circuit diagram of a three-phase full bridge uncontrolled diode rectifier.
- Draw the output voltage waveform, and output current waveform for one phase.
- Calculate the following parameters,
 - Mean value of the output voltage.
 - Output voltage ripple frequency.

(10 marks)

02.

- a) A single-phase fully controlled thyristor bridge rectifier is supplied 230 V, 50 Hz. The source inductance and the thyristor voltage drops are negligible. Assuming continuous conduction,
- Draw the circuit diagram of the above system.
 - When considering firing angle as 30° ,
 - Show the output voltage waveform.
 - Calculate the mean value of the output voltage.
 - Calculate the displacement factor.
 - If supply source inductance is 0.9 mH/line, redraw the output voltage waveform for a firing angle of 30° .
 - Calculate the overlap angle (μ) for a load current of 30 A and a firing angle of 30° .

(14 marks)

- b) A three-phase fully controlled thyristor bridge rectifier is supplied 400 V, 50 Hz three-phase AC power supply. The source inductance is negligible.
- Draw the circuit diagram of the above system.
 - Calculate the mean value of output voltage.
 - Calculate the voltage ripple frequency.

(6 marks)

03.

- a) List down two basic types of DC to AC inverters based on the operating source.
- (2 marks)
- b) Write down equations defining all terms for follows,
- Depth of Modulation
 - Carrier ratio
- (4 marks)
- c) A single-phase voltage source inverter (VSI) is operating with the supply side voltage of 220 Vdc.
- Draw the circuit diagram of the above system.

- ii. Considering VSI is in the operation of the square wave switching,
 - a. Draw the output voltage waveform.
 - b. Calculate the RMS value of the fundamental component of the output voltage.
- iii. Consider the VSI is in the operation of the square wave unipolar PWM switching with carrier ratio of 6 and depth of modulation of 80%.
 - a. Draw the unipolar PWM modulator circuit, considering carrier signal as V_C , reference signal as V_R and switching signals as S1, S2, S3, and S4.
 - b. Draw the output voltage waveform with an appropriate values of voltage magnitudes.
 - c. Calculate the RMS value of the fundamental component of the output voltage.

(14 marks)

04.

- a) Draw the circuit diagram and explain the functionality of the buck boost converter.

(4 marks)
- b) Draw following waveforms for buck boost converter considering converter is operating in a continuous conduction mode under the following conditions: input voltage $V_d = 100$ V, duty factor $D = 0.75$, output power $P_o = 600$ W inductance $L = 100$ μ H and $f_s = 400$ kHz. Assume ideal components.
 - i. Calculate the following parameters,
 - a. Output voltage
 - b. Output ripple current
 - c. Maximum output current
 - d. Input current. State any assumptions you made.
 - ii. Draw following waveforms,
 - a. Output voltage
 - b. Inductor voltage
 - c. Inductor current

(16 marks)

05.

- a) Explain the requirement of power electronics for High Voltage Direct Current (HVDC) transmission. (4 marks)
- b) List down two advantages of switching power supplies over linear power supplies. (4 marks)
- c) Provide the circuit diagram for flyback converter and explain the advantages of flyback converters. (4 marks)
- d) Draw the block diagram for a motor drive and list down basic two factors to vary the power electronic converter. (4 marks)
- e) Explain the working principle of the "Induction Heating" using examples. (4 marks)

----- End of the Paper -----