


**University of Ruhuna- Faculty of Technology**  
**Bachelor of Engineering Technology Honours Degree**  
**Level 2 (Semester II) Examination, December 2023**  
**Academic year 2021/2022**

Course Unit: ENT2213 Digital Electronic Systems

Time Allowed: 3 hrs

- All symbols have their usual meanings.
- Answer **all six(06)** questions.
- Use Annexure 1 and 2 to answer the relevant questions.

 - 1.
- a. The following circuit can operate as a two-level system that can generate HIGH and LOW states of output over a continuous input voltage. Briefly discuss the working principle of the following circuit generating HIGH and LOW logic states.  
 [2 marks]




- b. Write the decimal number 627 in following forms.
- i. Binary representation. [2 marks]
  - ii. Octal representation. [2 marks]
  - iii. Hexadecimal representation. [2 marks]
- c. Digital electronic is based on operating logical functions in binary representation of input signals and alphanumeric characters.
- i. What would you understand by the acronyms LSB and MSB in a 8-bits binary number. [1 mark]
  - ii. Briefly, discuss the need and the importance of Octal and Hexadecimal representations in digital electronics. [1 mark]

- 2.
- a. Define the terms "Combinational Logic" and the "Sequential Logic" in digital electronics.  
 [2 marks]
- b. Define the operation of the gates NOR, and NAND by writing the,
- i. Truth Table. [1 mark]
  - ii. Boolean expression. [1 mark]
- c. Sketch the logic circuit diagram for the following Boolean expression. [2 marks]


$$Y = A \cdot B + A \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{C}$$

- d. In digital electronic, the Active-High logic consider the High voltage state as logical True(T) state, whereas the Active-Low logic consider the High voltage state as logical False(F) state and vice-versa.  
Construct the truth table for following gates and express the function of logic gates in Active-High and Active-Low logic.  
(Note: Use the letter **T** for the **True** state and **F** for the **False** state. )

i. [2 marks]

 

ii. [2 marks]

 

3.

- a. Use Boolean Algebra to show that [4 marks]

$$A + B.C = (A + B).(A + C)$$

- b. Using the distributive law in part (a.) above, express the following equation in product of sum form with 4 product terms, each with a sum of 3 variables. [6 marks]


$$F = H + I.\bar{J} + \bar{K}.L$$

4. Implement the following Boolean function,

$$X = \bar{A}.\bar{B}.\bar{C} + B.\bar{C} + B.C$$

- using a 8:1 Multiplexer. [4 marks]
- using a 4:1 Multiplexer plus a NOT gate. [4 marks]
- using a 2:1 Multiplexer plus a NOT gate and an OR gate. [2 marks]

 
5. The following figure shows a 3-bit Asynchronous counter.



- a. Construct the timing diagram for the binary output of  $Q_0$ ,  $Q_1$  and  $Q_2$  and explain the working of the counter. Assume all the flip-flops are reset to 0 initially. [3 marks]  
**(Use the provided space in Annexure 1 to draw the timing diagram)**
  
- b. For an industrial application, it is required to count from 1 to 6 repeatedly. Drawing the circuit diagram, explain how you would modify the above 3-bit asynchronous counter for this purpose. (Note: Consider the D-flip-flops have active-High set and reset controllers.) [4 marks]
  
- c. The flip-flops have a propagation time delay. The propagation time delays of D-flip-flops are  $T_{PLH} = T_{PHL} \approx 12 \text{ ns}$  and the propagation time delays of basic logic gates are negligible.
  - i. What is the total propagation time delay of the above counter in part b. [2 marks]
  - ii. Calculate the maximum clock frequency that the above counter can be operated. [1 mark]

6.

 - a. In digital Electronics what do you understand by the term "Shift Register"? [1 mark]
- b. The following Figure shows a schematic circuit diagram of a Parallel In /Serial Out 4-bit shift register. Assume the flip flops are RESET initially.




- i. Describe the operation of the above circuit when the logic state of the SHIF/LOAD input is LOW(0) and HIGH(1). [2 marks]
- ii. Complete the following function table for the parallel data input of "1011" for D3, D2, D1 and D0 inputs respectively. [3 marks]

(Use the provided Table 6.b.ii. in Annexure 2)

Operation	CLOCK	input	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
CLEAR			0	0	0	0
SHIF/LOAD=0	↑	D <sub>0</sub> =1 D <sub>1</sub> =1 D <sub>2</sub> =0 D <sub>3</sub> =1				
SHIF/LOAD =1	↑					
	↑					
	↑					
	↑					

 - c. The following circuit shows the circuit diagram of a 4-bit Linear Feedback Shift Register (LFSR). S and R are Active-Low asynchronous set and reset controllers. Initially the flip-flop 1 (FF-1) is SET to HIGH(1) logic state and all the other flip-flops are RESET to LOW(0) logic state.

Describe the operation of the following LFSR by constructing the function table. [4 marks]




(Use the provided Table 6.c. in Annexure 2)

Operation	CLOCK	$Q_1$	$Q_2$	$Q_3$	$Q_4$
Initialize		1	0	0	0
CLOCK					

## Laws and Rules in Boolean Algebra

- |     |                                                      |   |                          |
|-----|------------------------------------------------------|---|--------------------------|
| 1.  | $X + 0 = X$                                          | } | OR operations            |
| 2.  | $X + 1 = 1$                                          |   |                          |
| 3.  | $X + X = X$                                          |   |                          |
| 4.  | $X + \overline{X} = 1$                               |   |                          |
| 5.  | $X \cdot 0 = 0$                                      | } | AND operations           |
| 6.  | $X \cdot 1 = X$                                      |   |                          |
| 7.  | $X \cdot X = X$                                      |   |                          |
| 8.  | $X \cdot \overline{X} = 0$                           |   |                          |
| 9.  | $\overline{\overline{X}} = X$                        |   | Double complement        |
| 10. | $X + Y = Y + X$                                      | } | Commutative laws         |
| 11. | $XY = YX$                                            |   |                          |
| 12. | $(X + Y) + Z = X + (Y + Z)$                          | } | Associative laws         |
| 13. | $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$          |   |                          |
| 14. | $X(Y + Z) = XY + XZ$                                 |   | Distribution Law         |
| 15. | $X + Y \cdot Z = (X + Y) \cdot (X + Z)$              |   | Dual of Distributive Law |
| 16. | $X + XZ = X$                                         | } | Laws of absorption       |
| 17. | $X(X + Z) = X$                                       |   |                          |
| 18. | $X + \overline{X}Y = X + Y$                          | } | Identity Theorems        |
| 19. | $X(\overline{X} + Y) = X \cdot Y$                    |   |                          |
| 20. | $\overline{X + Y} = \overline{X} \cdot \overline{Y}$ | } | De Morgan's Theorems     |
| 21. | $\overline{X \cdot Y} = \overline{X} + \overline{Y}$ |   |                          |

5. a. [3 marks]

 

6 b. ii. Function Table

Operation	CLOCK	input	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
CLEAR			0	0	0	0
SHIFT/LOAD=0	↑	D <sub>0</sub> =1 D <sub>1</sub> =1 D <sub>2</sub> =0 D <sub>3</sub> =1				
SHIFT/LOAD =1	↑					
	↑					
	↑					
	↑					

6 c. Function Table

Operation	CLOCK	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>
Initialize		1	0	0	0
CLOCK					