



## University of Ruhuna- Faculty of Technology

Bachelor of Engineering Technology Honours Degree

Level 1 (Semester II) Examination, Nov-Dec. 2023

Academic Year 2021/2022

Course Unit: **ENT1242 Electricity and Magnetism**


Duration: **2 hours**

---

Instructions and details:

- Answer all **Five (05)** questions.
- The paper carries a total of 100 marks and each question carries 20 marks.
- Calculators are allowed for calculations.
- When relevant, answers should be expressed in terms of the given (relevant) variables and simplified.
- All symbols have their usual meanings.
- $k = k_e = \frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ Nm}^2/\text{C}^2$ .
- $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$ .
- $\mu_0 = 4\pi \times 10^{-7} \text{ T.m/A}$ .

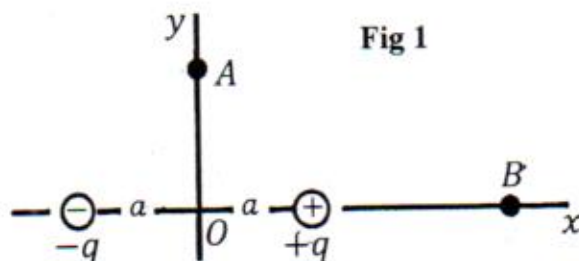1. As shown in Figure 1, an electric dipole is made of two charges of equal magnitude  $q$  and opposite signs that are separated by a distance  $2a$ . The dipole is located along the  $x$ -axis and it is centered at the origin  $O$  of the  $xy$  coordinate system. Let  $k$  denote the Coulomb's constant.




- (a) Find the electric field ( $\vec{E}$ ) of the dipole at point  $A(0, y)$  on the  $y$ -axis, in unit-vector notation.  
 (\*Hint/s: You may want to draw the fields. The field due to a point charge:  $\vec{E} = k \frac{|q|}{r^2} \hat{r}$ )
- (b) Find the electric potential ( $V$ ) at point  $B(x, 0)$  on the  $x$ -axis as shown in the Figure.

If the point  $B(x, 0)$  is located far-away from the dipole (i.e.  $x \gg a$ ) then,

- (c) Find the approximate potential at point  $B$ . [\*Hint/s: part-(b)]
- (d) Find the approximate electric field at point  $B$  in the positive  $x$  direction. [\*Note/s: Use the result of part-(c).  $\frac{d}{dx} x^n = nx^{n-1}$  ]


2.

- (i) In Figure 2, a charged parallel-plate capacitor is made of plates of area  $A$  and plate separation  $d$ . If the uniform electric field between the plates is  $E = \sigma/\epsilon_0$  then, find the capacitance ( $C$ ) of the capacitor in terms of  $\epsilon_0$ ,  $A$  and  $d$ , where  $\sigma$  is the magnitude of the surface charge density of each plate. (\*Hint/s: First you may want to show that the potential difference between the plates is  $|\Delta V| = Ed$ , and then consider the definition of capacitance using charge  $Q$ .)

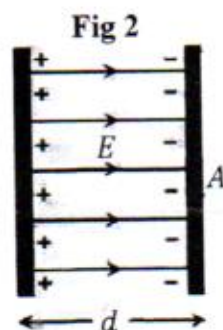

- (ii) Capacitors of capacitances  $C_1 = C_2 = 20 \mu\text{F}$  and  $C_3 = C_4 = 30 \mu\text{F}$  are connected in a capacitor network as shown in Figure 3.

Fig 3

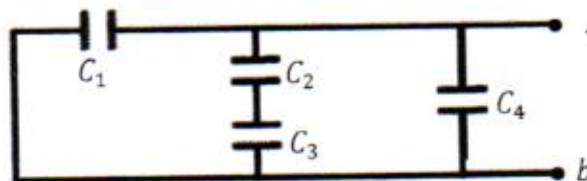


A potential difference of 10 V is applied between the points  $a$  and  $b$ . Then,

- (a) Calculate the equivalent capacitance ( $C_{eq}$ ), between the points  $a$  and  $b$ .
- (b) Calculate the energy ( $U$ ) stored in the capacitor network.

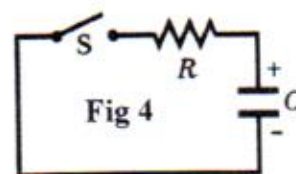- (iii) An  $RC$  series circuit is shown in Figure 4. The initial charge in  $C$  is  $Q_0$ . The switch  $S$  is turned on at time  $t = 0$ , so that  $C$  discharges. Then, show that the charge of the capacitor at time  $t$  can be written as

$$q = Q_0 e^{-\frac{t}{RC}}$$

- (\*Hint/s: Current  $i = -\frac{dq}{dt}$ . The solution for the differential equation  $\frac{dq}{dt} + bq = 0$  can be written as  $q = ae^{-bt}$ , where  $a$  and  $b$  are constants.)





3. In the circuit in Figure 5, the resistances of the resistors are  $R_1 = R_5 = 200 \Omega$ ,  $R_3 = 400 \Omega$ ,  $R_2 = R_4 = 800 \Omega$  and the ideal emfs of the batteries are  $\varepsilon_1 = 5.00 \text{ V}$  and  $\varepsilon_2 = 10.0 \text{ V}$ .

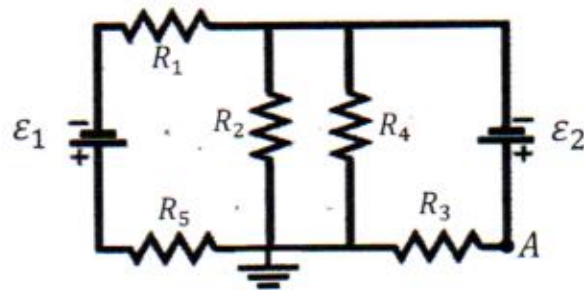


Fig 5

- Calculate the current flowing through  $R_1$ . (\*Hint/s: first you may want to reduce, simplify & redraw the circuit. Kirchoff's rules.)
  - Calculate the current flowing through  $R_2$ .
  - Calculate the current flowing through  $R_3$ .
  - Mention whether the battery  $\varepsilon_2$  is being charged or discharged. Briefly give your reasons.
  - If one point of the circuit is grounded as shown then, calculate the electric potential at point A.
  - Calculate the power dissipated by  $R_3$ .
  - Calculate the potential difference across  $R_2$ .
- 4.
- An ideal long solenoid inductor has  $n$  number of turns per unit length and carries a current  $i$ . Then,

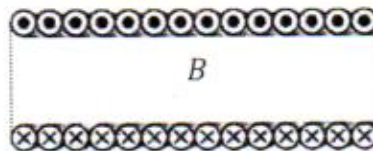


Fig 6

- Show that the uniform magnetic field generated inside the solenoid can be written as
 
$$B = \mu_0 i n.$$
 Note/s: See Figure 6. Use Ampere's law.
  - If the solenoid has a length  $l$  and a circular cross-sectional area  $A$  then, find its inductance ( $L$ ).
  - If a straight wire of length  $l_0$  carrying a current  $i$  is placed at the center of the solenoid perpendicular to its central axis then, find the magnitude of the magnetic force ( $F$ ) on the wire.
- A uniform magnetic field of magnitude  $B$  is perpendicular to the plane of a circular wire loop of radius  $r$ . If the loop has a resistance  $R$  then, find the rate at which  $B$  must be changed to induce a current  $i$  in it. [i.e. find  $\left| \frac{dB}{dt} \right|$ . \*Hint/s: Ohm's law, Faraday's law]
  - A current  $i$  flows through a  $10 \text{ H}$  inductor. If an emf of  $50 \text{ V}$  is produced across it then, calculate the rate of change of the current. [i.e. calculate  $\left| \frac{di}{dt} \right|$ .]

5.

- (i) As shown in Figure 7, an inductor  $L = 6.0 \mu\text{H}$  is connected in series with a resistor  $R = 1.0 \text{ k}\Omega$ . The emf of the battery is  $\mathcal{E} = 12 \text{ V}$ . The switch  $S$  is turned on at time  $t = 0$ . Then, for the circuit
- (a) Find the time constant. (i.e. the inductive  $\tau$ )
- (b) Find the current ( $i$ ) at time  $t = 6.0 \text{ ns}$ . [\*Hint/s:  $i = i_{\text{max}}(1 - e^{-\frac{t}{\tau}})$ , where  $e = 2.72$ ]

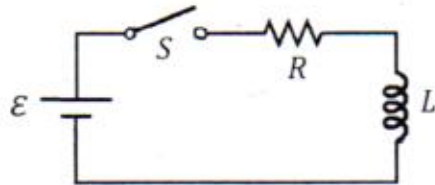


Fig 7

- (ii) In Figure 8, an  $RLC$  circuit is made of a resistor  $R = 180 \Omega$ , a capacitor  $C = 100 \mu\text{F}$ , an inductor  $L = 240 \text{ mH}$ , and a driving emf  $\mathcal{E}$  that are connected in series.  $\mathcal{E}$  has an amplitude of  $\mathcal{E}_m = 40.0 \text{ V}$  and a frequency of  $f_d = 50.0 \text{ Hz}$ .

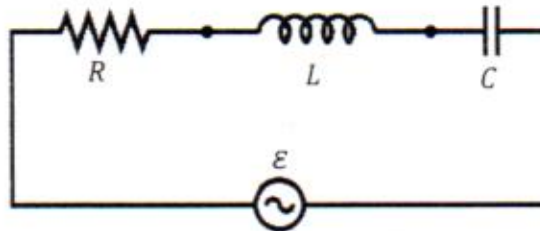


Fig 8

For the circuit,

- (a) Calculate the reactance of  $C$ . [\*Hint/s:  $X_L = \omega_d L$ ,  $X_C = 1/(\omega_d C)$ ]
- (b) Calculate the reactance of  $L$ .
- (c) Calculate the impedance ( $Z$ ).
- (d) Calculate the phase angle ( $\phi$ ).
- (e) Calculate the RMS current. [\*Hint/s: You may want to first calculate the current amplitude]
- (f) Calculate the average rate at which energy is dissipated.
- (g) Calculate the power factor.

@@@@@@@@@@@@@@@@@@