

UNIVERSITY OF RUHUNA

BACHELOR OF SCIENCE SPECIAL DEGREE LEVEL I (Semester II)
EXAMINATION DECEMBER- 2017

Subject: PHYSICS

Course unit: PHY4112, Electronics II

TIME: 02 hours

Answer FOUR (04) questions only

Q1.

- a) Design a logic circuit that has three inputs, A, B and C, and which will produce HIGH output only when two or more inputs are HIGH.

[07 marks]

- b) In an audio CD, the audio voltage signal is typically sampled about 44,000 times per second, and the value of each sample is recorded on the CD surface as a binary number. The each recorded binary number represents a single point on the audio signal wave form.

- i. If the binary numbers are six bits in length, how many different voltage values can be represented by a single binary number? Repeat for eight bits and ten bits.
- ii. If ten-bit numbers are used, how many bits will be recorded on the CD in one second?
- iii. If a CD-ROM can store 650 megabytes, how many seconds of audio can be recorded when ten-bit numbers are used (mega = 2^{20}).

[09 marks]

- c) The movement of binary data and codes from one location to another is the most frequent operation performed in a digital system.

- i. What is the major cause of error in transmission process?
- ii. Why this error is significant?
- iii. Briefly discuss the parity method in detecting the error code.

[09 marks]


- Q2. Digital systems obtain binary coded data and information that are continuously being operated on in some manner like decoding and encoding, multiplexing and demultiplexing etc.

- i. What are the functions of decoder and encoder?
- ii. Discuss an application of a priority encoder.
- iii. Using Karnaugh map or other method design logic circuit diagram for 4-input priority encoder (4 to 2 line priority encoder).
- iv. What are the functions of multiplexer and demultiplexer?
- v. Giving relevant gate combinations explain the function of a circuit of two-input multiplexer.


[25 marks]

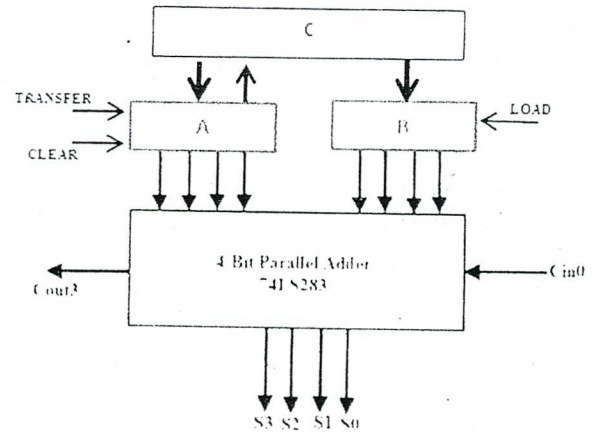Q3.

Several parallel adders are available as ICs. The most common is four-bit parallel adder, illustrated in the figure. All the bits of A and B are fed into the adder circuits simultaneously and therefore parallel addition is very fast.



 - Construct logic circuit diagram for a single bit full adder circuit.
- What are A, B and C circuits of the given full adder?
- Write down the sequence of operation of the complete adder by following the given timing diagram.




- What is the main cause of delay in an adder circuit and what remedy has been used in this circuit to overcome the delay?
- Draw necessary modification to perform subtraction operations using the same circuit.

[25 marks]

 Q4.

Clocked flip-flops are versatile devices that can be used in variety of applications including frequency division and counting. Figure shows the wiring arrangement of two J-K flip-flops to form a two bit binary counter.



 - Extend the flip-flop arrangement for 3-bit asynchronous (ripple) up counter.
 - What is meant by up counters and down counters and what changes has to be taken to convert this to down counter?
 - By drawing all waveforms explain the operation of a 3-bit up counter.
 - Write down all possible counting operations for 3-bit up counter.
 - Modify the same counter to perform the counting operations only between 2 and 5.

[18 marks]

Continue to next page..

b)

- i. Design a logic circuit for 3-bit synchronous up counter.
- ii. "Counting operations of synchronous counters are stable than asynchronous counters". Explain this statement briefly.

[07 marks]

Q5.

a) Discuss **any two** of the following Flip-Flop applications.


- i. Flop-Flop synchronizations
- ii. Detecting the input sequence
- iii. Serial data transfer

[05 marks]


b) Use same sheet to answer this question and attached with your answer scripts.

Complete the output wave forms of given flip-flops (i to v) according to their inputs.



i.

 



ii.

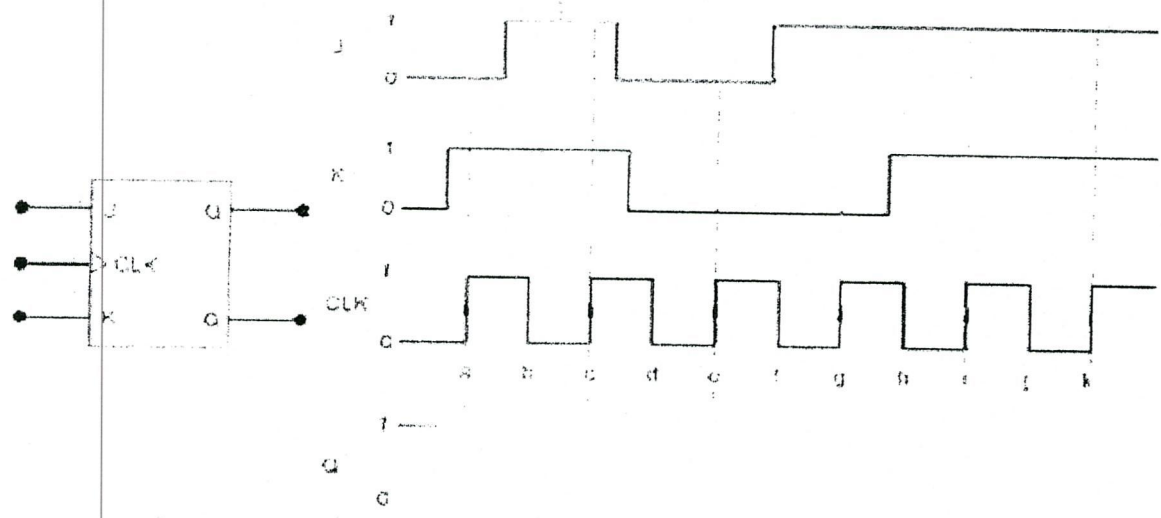



iii

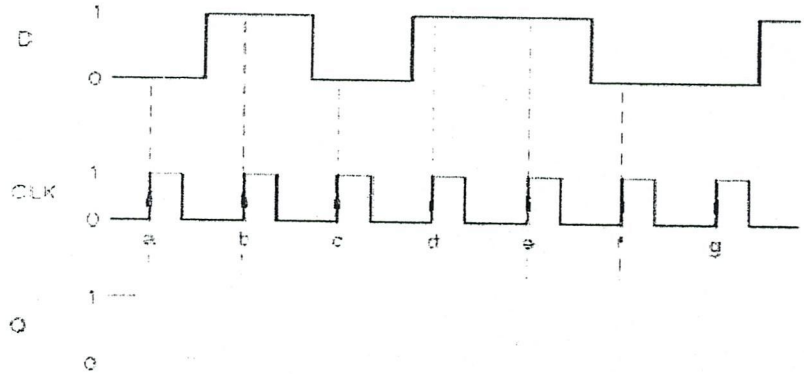 

iv

  

v

  

(Note: Quasi stable interval is 2 ms ($>$ width of the clock pulse) for **both** cases)

[20 marks]