



UNIVERSITY OF RUHUNA

Faculty of Engineering

End-Semester 1 Examination in Engineering: October 2019

Module Number: EE1302 Module Name: Introduction to Electrical Engineering

[Three Hours]

[Answer all questions, each question carries ten marks]

- Q1 a) i) Explain what a "super node" is with regard to nodal analysis in dc circuits.
 ii) Find the node voltages of the non-reference nodes of the dc circuit shown in Figure Q1 (a) by using nodal analysis.
 iii) Hence or otherwise find the current I_0 shown in Figure Q1 (a).

[5 Marks]

- b) i) State Thevenin's theorem with regard to dc circuit analysis.
 ii) Find the Thevenin's equivalent circuit across the terminals a and b of the circuit shown in Figure Q1 (b) removing the load resistance R_L .
 iii) Hence, find the load current if a $R_L = 8 \text{ k}\Omega$ load resistor is connected across the terminals a and b .

[5 Marks]

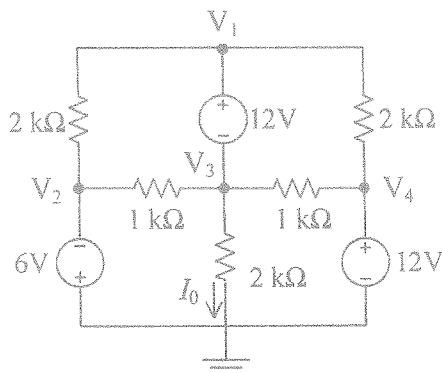


Figure Q1 (a)

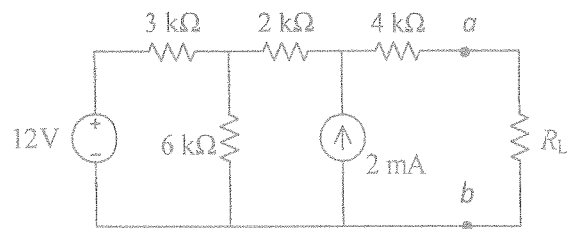


Figure Q1 (b)

- Q2 a) i) Briefly explain the time constant of RL and RC circuits.
- ii) The switch in the series connected RL dc circuit shown in Figure Q2 (a) closes at $t = 0$. Show that the total response of the inductor current $i(t)$ can be given as

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

where $i(0)$ and $i(\infty)$ are the initial and final values of the inductor current and τ is the time constant of the circuit, respectively.

- iii) The switch of the circuit shown in Figure Q2 (b) has been closed for a long time. It opens at $t = 0$. Find $i(t)$ for $t > 0$.

[5 Marks]

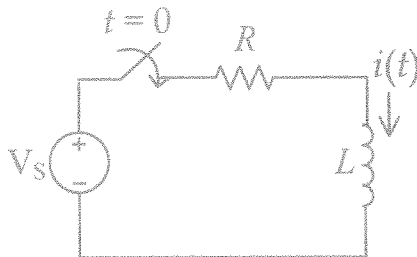


Figure Q2 (a)

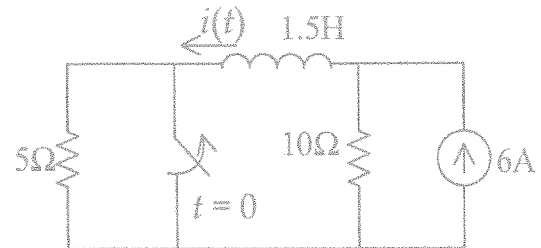


Figure Q2 (b)

- b) The switch of the RLC circuit shown in Figure Q2 (c) has been closed for a long time. It opens at $t = 0$.
- i) Check whether the circuit is underdamped, over damped, critically damped or un-damped and justify your answer.
- ii) Find the total response of the capacitor voltage $v(t)$ for $t > 0$.
- iii) Hence or otherwise find the inductor current $i(t)$ for $t > 0$.

[5 Marks]

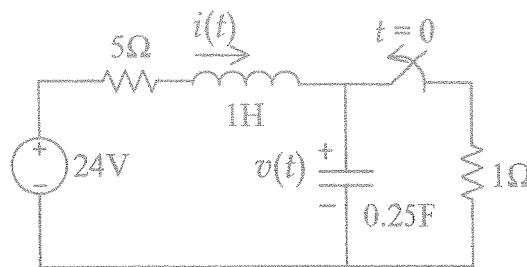


Figure Q2 (c)

- Q3 a) A single phase ac voltage is given by $v(t) = V_p \sin(\omega t)$. Show that the;
- i) Half cycle average voltage is $2V_p/\pi$.
- ii) RMS voltage is $V_p/\sqrt{2}$.
- iii) Form factor of the voltage waveform is 1.11.
- iv) Peak factor of the voltage waveform is 1.414.
- Note: $\cos 2\theta = 1 - 2\sin^2\theta$

[4 Marks]

- b) i) Find the phase angle between the two currents $i_1 = -4 \sin(377t + 55^\circ)$ and $i_2 = 5 \cos(377t - 65^\circ)$.
- ii) Does i_1 lag or lead i_2 ?

$$\text{Note: } \sin(\theta \pm 90^\circ) = \pm \cos \theta \quad \sin(\theta \pm 180^\circ) = -\sin \theta$$

$$\cos(\theta \pm 90^\circ) = \mp \sin \theta \quad \cos(\theta \pm 180^\circ) = -\cos \theta$$

[2 Marks]

- c) i) Find the phasor domain equivalent circuit of the ac circuit shown in Figure Q3.
- ii) Hence or otherwise, find the instantaneous source current $i_s(t)$ of the circuit.

[4 Marks]

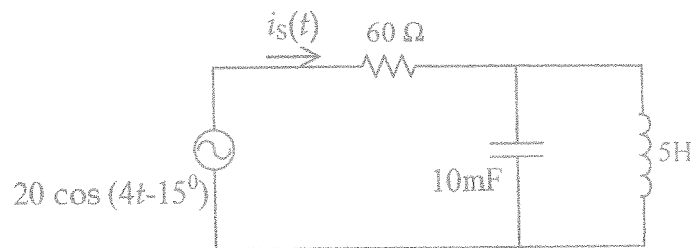


Figure Q3

- Q4 a) The current $i(t)$ drawn by a series connected single phase load and the applied voltage $v(t)$ are given by

$$i(t) = 4 \cos(100\pi t + 10^\circ) \text{ A}$$

$$v(t) = 120 \cos(100\pi t - 20^\circ) \text{ V.}$$

- i) Find the real power, reactive power and the apparent power drawn by the load.
- ii) Calculate the power factor of the load.
- iii) Determine the load impedance and the values of the elements that form the load.
- iv) Calculate the value of the element to be connected in parallel with the load in order to bring the overall power factor to 0.95 lagging.

[5 Marks]

- b) Three equal impedances, $60 + j30\Omega$ each, are delta connected and connected to a 230 V three phase supply. Another three equal impedances, $40 + j10\Omega$ each are star connected across the same circuit at the same points. Determine;

- i) The line current.
- ii) The total complex power supplied to the two loads.
- iii) Overall power factor of the combined load.

[5 Marks]

- Q5 a) i) State are three most common types of faults that occur in a domestic wiring system?
- ii) Various protective mechanisms are employed to safeguard the consumer and the equipment in an electrical installation. What are the favorable characteristics of a protective equipment used in an electrical installation?
- iii) Briefly explain the operation of a Miniature Circuit Breaker (MCB) during a short circuit and over loading faults.
- iv) What are the basic elements available in a domestic wiring system up to the distribution box? Draw a sketch showing how they are connected.

[5 Marks]

- c) Suppose you are asked to measure the current and the voltage across the resistor R_1 in the circuit shown in Figure Q5. You are given an ammeter with internal resistance R_a and a voltmeter with internal resistance R_v .

- i) On separate figures, show how you connect the ammeter and the voltmeter for measuring the current through the resistor R_1 and the voltage across R_1 .
- ii) Derive expressions for the voltage across the resistor R_1 in terms of V, R_1, R_2 and R_v with and without the voltmeter connected to the circuit. From these expressions, what can be said about the construction of a voltmeter and the accuracy of the voltage measurement?
- iii) Explain how a galvanometer with $100\mu\text{A}$ full scale and $50\ \Omega$ internal resistance be converted to a multi-range ammeter with 3-full scales of $0.5\text{A}, 2\text{A}$ and 5A .
- iv) Draw a circuit diagram of the suggested multi-range ammeter in part iii).

[5 Marks]

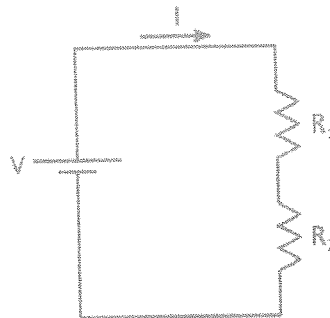


Figure Q5