



# UNIVERSITY OF RUHUNA

## Faculty of Engineering

End-Semester 3 Examination in Engineering: August 2018

Module Number: EE3301

Module Name: Analog Electronics

[Three Hours]

[Answer all questions, each question carries 10 marks]

All notations have their usual meanings.

Q1 a) Figure Q1 a) shows the monolithic IC construction of two electronic components. Name the components.

[1 Mark]

b) The conventional discrete bias circuit in Integrated Circuit design using the voltage divider method is shown in Figure Q1 b). Show that this circuit is equivalent to a constant current source in series with a load by deriving an expression for the current.

[3 Marks]

c) i) Reproduce the circuit of an ideal differential amplifier that has collector bias resistors of  $7\text{ k}\Omega$ , a supply voltage of  $+18\text{ V}$ , a constant current source of  $2\text{ mA}$  and designate the input and output terminals.

ii) Calculate the internal emitter resistance of the transistors for this ideal differential amplifier.

iii) When the input 2 of the ideal differential amplifier circuit is grounded and a sinusoidal signal is applied to the input 1, calculate the magnitude and phase of the voltages at the

I) emitters of the transistors.

II) output 1.

iv) When the signals  $\pm 15 \sin(\omega t)\text{ mV}$  are applied simultaneously to inputs 1 and 2, by inference determine the magnitude and phase of the two output voltages.

[6 Marks]

Q2 a) List five (05) important characteristics of an operational amplifier (Op-Amp).

[2 Marks]

b) Figure Q2 b) shows the packaging and pin configurations for a Texas Instruments  $\mu 741$  Op-Amp. The pin identification and related functions are

1 - Offset Null

5 - Offset Null

2 - IN-

6 - OUT

3 - IN+

7 -  $V_{cc+}$

4 -  $V_{cc-}$

8 - NC

Match the pin identifications to Figure Q2 b) and state the meaning of each function.

[2 Marks]

- c) For an Op-Amp define the
- frequency response,
  - gain bandwidth product (GBP) and
  - slew rate.

[1.5 Marks]

- d) The output offset voltages of an Op-Amp are due to the input bias or offset currents and input offset voltages.

Using Figure Q2 d), perform an analysis to calculate a value for the compensating resistor  $R_c$  that minimizes the output offset voltage only due to the input offset currents.

[4.5 Marks]

- Q3 a) Synthesize a circuit using two operational amplifiers to obtain the difference between two voltages without restrictions.

[Hint : Invert one input and add to the other input]

[2 Marks]

- b) i) Describe an ideal operational amplifier circuit to integrate a sinusoidal input signal  $v_{in} = E \sin(\omega t)$  and derive expressions for the output voltage and its frequency.
- ii) Explain modifications to the circuit in practice and the reasons for it.
- iii) Sketch the frequency response of a practical operational amplifier integrator and identify the integration region.

[4 Marks]

- c) i) Filters are classified according to their order. State the relevance of the order to the filter response and its fall off.
- ii) Filters are also classified according to their specific design. State the two most common design types.
- iii) Describe the difference between these two types in part (ii) by considering their response characteristics.

[4 Marks]

- Q4 a) State the difference between an oscillator and a multivibrator.

[1 Mark]

- b) State the Barkhausen criterion for a system to oscillate.

[1.5 Marks]

- c) Figure Q4 c) shows the circuit of a Wien Bridge oscillator.  $Z_1$  is a network with a capacitor  $C_1$  in series with a resistor  $R_1$  and  $Z_2$  is a network with a capacitor  $C_2$  in parallel with a resistor  $R_2$ . Calculate the

- feedback ratio  $\beta$ .
- oscillator frequency  $\omega$ .
- required amplifier gain, if the resistors and capacitors have the same value.

[4 Marks]

d) Figure Q4 d) shows the circuit of an astable multivibrator using an operational amplifier as a comparator. Assume that the output voltages of the comparator are equal in magnitude and opposite in polarity  $\pm V_{max}$ . Assume also that the output is at  $+V_{max}$ .

- i) State a value for the feedback ratio  $\beta$ .
- ii) Explain the charge characteristics for the capacitor with a graph.
- iii) Using the graph in part ii), find the output of the circuit.

[3.5 Marks]

- Q5 a)
- i) State two differences between a JFET (Junction Field Effect Transistor) and a BJT (Bipolar Junction Transistor).
  - ii) Sketch the structure of a N-channel JFET showing the DC biasing for active mode operation in common source configuration (Clearly indicate the terminals, the depletion region and the channel of conduction).
  - iii) Reproduce the N-channel depletion type MOSFET (Metal Oxide Semiconductor FET) drain characteristics clearly indicating the different regions of the curve.

[3 Marks]

- b) i) Reproduce the transfer characteristic curve for a N-channel JFET.
- ii) Show that the transconductance ( $g_m$ ) for a JFET is given by,

$$g_m = \frac{2I_{DSS}}{|V_P|} \sqrt{\frac{I_D}{I_{DSS}}} \quad \text{Seimens}$$

[Hint: Use the transfer characteristic curve produced in part b) i).

[2 Marks]

c) The JFET in the common source amplifier circuit shown in Figure Q5 c) has  $I_{DSS} = 12 \text{ mA}$ ,  $V_P = (-4) \text{ V}$  and  $r_d = 100 \text{ k}\Omega$ .

- i) Find the Q point values of  $I_D$  and  $V_{DS}$  and confirm that the Q point is in the active region.
- ii) Find the value of transconductance ( $g_m$ ).
- iii) Draw the small signal ac equivalent circuit for the common source amplifier and find the voltage gain.

[5 Marks]

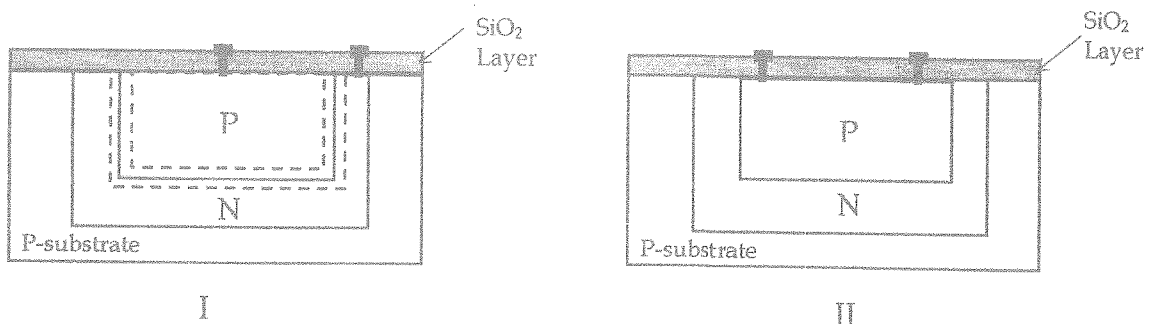


Figure Q1 a)

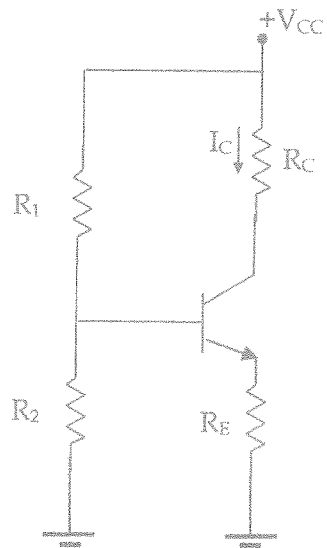


Figure Q1 b)

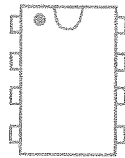


Figure Q2 b)

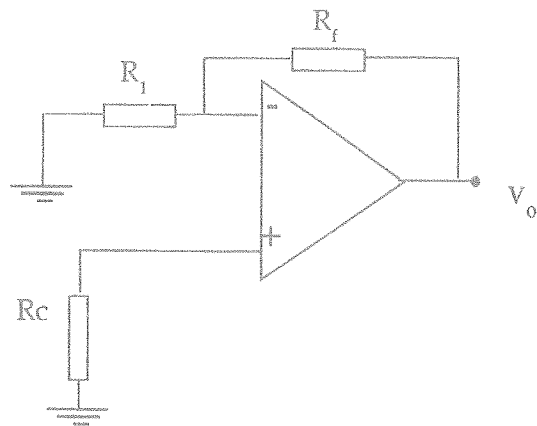


Figure Q2 d)