



UNIVERSITY OF RUHUNA

Faculty of Engineering

End-Semester 8 Examination in Engineering: December 2018

Module Number: EE8209

Module Name: Microwave Communication

[Three Hours]

[Answer all questions, each question carries 10 marks]

- Q1 The transmission line circuit in the Figure Q1 has $V_g = 15 \text{ V}_{\text{rms}}$, $Z_g = 75 \Omega$, $Z_0 = 75 \Omega$, $Z_L = 60 - j40 \Omega$, and $l = 0.7\lambda$. Compute the power delivered to the load using three different techniques:
- a) Find Γ and compute $P_L = \left(\frac{V_g}{2}\right) \frac{1}{Z_0} (1 - |\Gamma|^2)$; [2.5 Marks]
- b) Find Z_m and compute $P_L = \left| \frac{V_g}{Z_g + Z_m} \right|^2 \text{Re}\{Z_m\}$; [2.5 Marks]
- c) Find V_L and compute $P_L = \left| \frac{V_L}{Z_L} \right|^2 \text{Re}\{Z_L\}$; [2.5 Marks]
- d) Discuss the rationale for each of these methods. Which of these methods can be used if the line is not lossless? [2.5 Marks]
- Q2 a) Derive the telegrapher equations for the T -model of a transmission line shown in Figure Q2.a. [4 Marks]
- b) For the parallel plate line shown in the Figure Q2.b, derive the R , L , G , and C parameters. Assume $W \gg d$. [3 Marks]
- c) For the parallel plate line of Problem Q2.b, derive the telegrapher equations using the field theory approach. [3 Marks]
- Q3. a) Write short notes regarding intrinsic impedance, wave impedance and characteristic impedance. [3 Marks]
- b) A radio transmitter is connected to an antenna having an impedance $80 + j40 \Omega$ with a 50Ω coaxial cable. If the 50Ω transmitter can deliver 30 W when connected to a 50Ω load, how much power is delivered to the antenna? [3 Marks]
- c) A generator is connected to a transmission line as shown in the accompanying Figure Q3. Find the voltage as a function of z along the transmission line. Plot the magnitude of this voltage for $-l \leq z \leq 0$. [4 Marks]

Q4 a) Derive the $[Z]$ and $[Y]$ matrices for the two-port networks shown in the Figure Q4. [5 Marks]

b) Consider a two-port network, and let $Z_{SC}^{(1)}, Z_{SC}^{(2)}, Z_{OC}^{(1)}$ and $Z_{OC}^{(2)}$ be the input impedance seen when port 2 is short-circuited, when port 1 is short-circuited, when port 2 is open-circuited, and when port 1 is open-circuited, respectively. Show that the impedance matrix elements are given by,

$$Z_{11} = Z_{SC}^{(1)}, Z_{22} = Z_{OC}^{(2)}, Z_{12} = Z_{21} = (Z_{OC}^{(1)} - Z_{SC}^{(1)})Z_{OC}^{(2)} \quad [5 \text{ Marks}]$$

Q5 a) A two-port network is known to have the following scattering matrix:

$$[S] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

i Determine if the network is reciprocal and lossless. [2 Marks]

ii If port 2 is terminated with a matched load, what is the return loss seen at port 1? [4 Marks]

iii If port 2 is terminated with a short circuit, what is the return loss seen at port 1? [4 Marks]

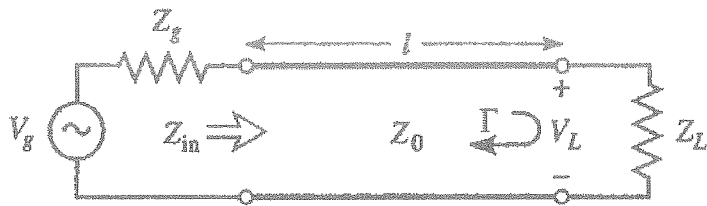


Figure Q1: The transmission line circuit

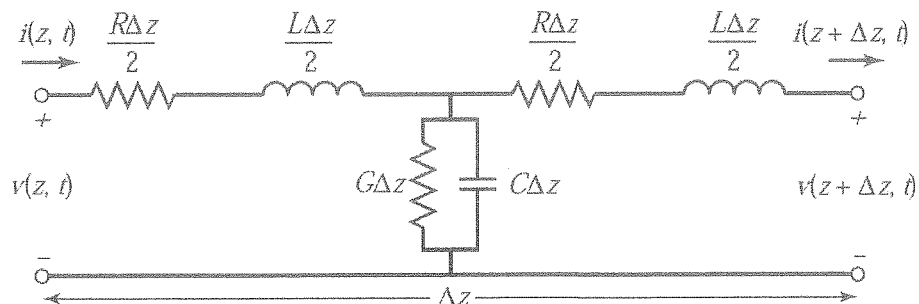


Figure Q2.a: Lumped element equivalent circuit for transmission line.

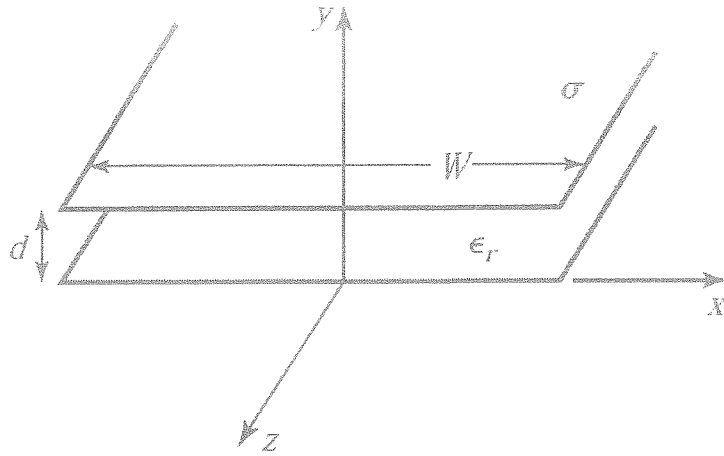


Figure Q2.b: The parallel plate line

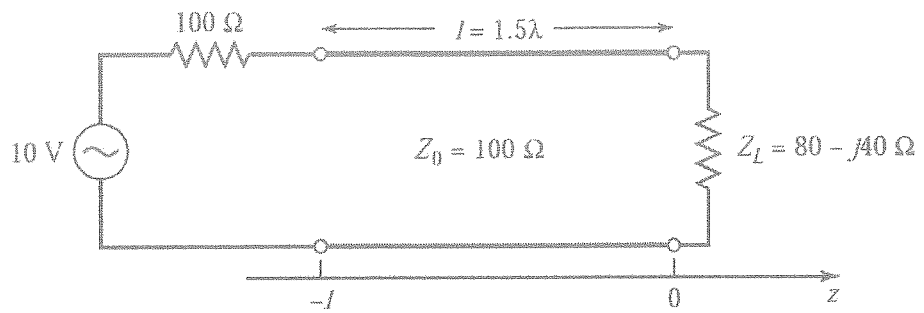


Figure Q3: Transmission line

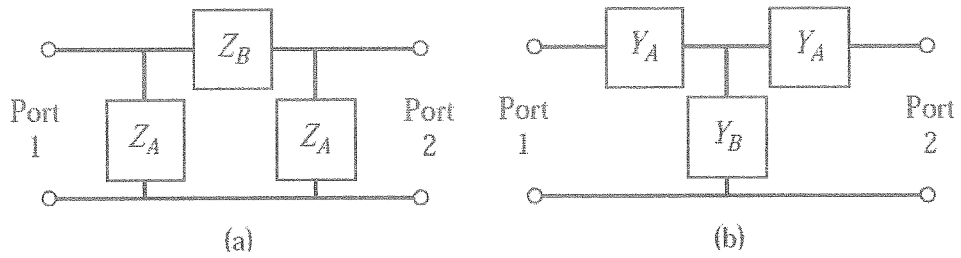


Figure Q4: Two port networks