



# UNIVERSITY OF RUHUNA

Faculty of Engineering

End-Semester 3 Examination in Engineering: July 2016

Module Number: EE3301

Module Name: Analog Electronics

[Three Hours]

[Answer all questions, each question carries 10 marks]

All notations have their usual meanings.

- Q1 a) Predict that the constant current source  $I$  in the circuit in Figure Q1 is mirrored to the collector current of the transistor T2. Assume that T1 and T2 are matched. [2 Marks]
- b) i) Reproduce the circuit of an ideal differential amplifier that has collector bias resistors  $6\text{ k}\Omega$ , supply voltage  $+15\text{ V}$  and a constant current source of  $2\text{ mA}$ .  
ii) Calculate the internal emitter resistance of the transistors for this ideal differential amplifier.  
iii) When the input 2 of the ideal differential amplifier circuit is grounded and a sinusoidal signal is applied to the input 1, calculate the magnitude and phase of the voltages at the  
I) emitters of the transistors  
II) output 1  
iv) When the signals  $\pm 20 \sin(\omega t)\text{ mV}$  is applied to inputs 1 and 2 respectively, by inference determine the magnitude and phase of the two output voltages. [6 Marks]
- c) The CMRR is defined as  $|A_d| / |A_{cm}|$  where  $A_d$  is the output difference voltage caused by common mode signals and  $A_{cm}$  the common mode signal respectively.  
i) State the meaning of the acronym CMRR.  
ii) When the inputs to a differential amplifier are:  
 $v_{i1} = 0.1 \sin(\omega t)$  and  $v_{i2} = -0.1 \sin(\omega t)$   
the outputs are:  $v_{o1} = -5 \sin(\omega t)$  and  $v_{o2} = 5 \sin(\omega t)$   
When both inputs are  $2 \sin(\omega t)$  the outputs are:  
 $v_{o1} = -0.04 \sin(\omega t)$  and  $v_{o2} = 0.04 \sin(\omega t)$   
Calculate the CMRR in dB. [2 Marks]

 


Figure Q1

- Q2 a) i) Define the properties of an ideal operational amplifier.  
 ii) Draw the circuit of an inverting amplifier based on an operational amplifier.  
 iii) State how the inverting amplifier can be used as a Voltage Follower.  
 iv) Explain briefly how a Voltage Follower can be used practically. [2 Marks]
- b) For an operational amplifier  
 i) Sketch the desired frequency response of the open loop gain and denote its characteristic features.  
 ii) Define the Gain Bandwidth Product (GBP) and the Closed Loop Gain Bandwidth ( $BW_{CL}$ ) in terms of the GBP.  
 iii) Define the slew rate.  
 iv) For a sinusoidal output  $V_o(t) = K \sin(\omega t)$ , predict the maximum frequency permitted by the slew rate. [2.5 Marks]
- c) For the inverting amplifier in part a), a resistor  $R_c$  can be connected in series with the non-inverting input in order to minimize the input offset current.  
 i) Formulate an expression for the value of  $R_c$ .  
 ii) Show that the output offset voltage due to bias currents are minimized when the input bias currents  $I_{B^+}$  and  $I_{B^-}$  are equal.  
 iii) Describe the origin of the input offset voltage and formulate an expression for the output offset voltage due to the input offset voltage.  
 iv) Express the total output offset voltage for the worst case from the derived expressions.  
 v) State how the output offset voltage is minimized in practice. [5.5 Marks]

- Q3 a) State the difference between an oscillator and a multivibrator. [0.5 Marks]
- b) Sketch a block diagram of an oscillator and state the necessary conditions for oscillation. [1 Mark]
- c) Figure Q3 c) shows the Colpitts oscillator circuit.  $R_1 \gg X_{C2}$  where  $X_{C2}$  is the reactance of  $C_2$ . Determine the oscillating frequency of the circuit and the gain required for the amplifier. [4 Marks]
- d) Explain the difference between a Butterworth and a Chebyshev filter considering their frequency responses. [1 Mark]
- e) Using the data in Table 1 and the circuit in Figure Q3 e), design a second-order low pass Butterworth filter with a cut-off frequency 2.5 kHz and a gain in the passband of 2. The constant  $K = 10^{-4}/(fC)$  where  $f$  is the desired cut-off frequency in Hz and  $C$  is the value of capacitance selected in Farads. [3.5 Marks]

 


Figure Q3 c)

 


Figure Q3 e)

Table 1

Table 14-1  
VCVS Filter Components

	$R_1$	$R_2$	$R_3$	$R_4$	$C_1$	$C_2$
Low-Pass Filter	$R_1$	$R_2$	$R_3$	$R_4$	$C_1$	$C_2$
High-Pass Filter	$C_1$	$C_2$	$R_3$	$R_4$	$R_1$	$R_2$

Table 14-2  
Second-Order Low-Pass Butterworth VCVS Filter Designs

Class	1	2	3	4	5	6
$R_1$	1.432	1.126	0.824	0.617	0.521	0.462
$R_2$	5.299	2.250	1.317	2.051	3.429	2.342
$R_3$	Open	6.752	3.128	3.203	3.572	2.560
$R_4$	0	6.752	3.444	16.012	22.602	32.034
$C_1$	0.132	0	0	0	0	0
$C_2$	0	0	0	0	0	0

\* Resistances in kilohms for a  $K$  parameter of 1.

Table 14-3  
Second-Order Low-Pass Chebyshev VCVS Filter Designs (2 dB)

Class	1	2	3	4	5	6
$R_1$	2.328	1.980	1.641	0.796	0.644	0.561
$R_2$	15.220	1.829	1.348	1.987	2.528	2.782
$R_3$	Open	7.829	3.529	3.292	3.466	2.670
$R_4$	0	7.829	9.950	16.460	24.261	31.601
$C_1$	0.14	0	0	0	0	0
$C_2$	0	0	0	0	0	0

\* Resistances in kilohms for a  $K$  parameter of 1.

Table 14-4  
Second-Order High-Pass Chebyshev VCVS Filter Designs (2 dB)

Class	1	2	3	4	5	6
$R_1$	0.640	1.320	2.117	2.625	3.040	3.299
$R_2$	3.299	1.660	0.985	0.794	0.626	0.513
$R_3$	Open	3.000	3.113	0.953	0.796	0.681
$R_4$	0	3.000	1.999	0.763	0.626	0.513

\* Resistances in kilohms for a  $K$  parameter of 1.

Source: Reprinted from *Rapid Practical Design of Active Filters*, D. Johnson and J. Hilburn, Copyright © 1975, John Wiley and Sons, Inc., by permission of John Wiley and Sons, Inc.

- Q4 a) i) Draw a circuit based on a single operational amplifier to subtract two signals  $V_1$  and  $V_2$  and formulate an expression for the output  $V_o$ .  
 ii) Give an alternative circuit to perform subtraction of two input signals and demonstrate the subtraction process. [4 Marks]
- b) i) Give an operational amplifier based ideal integrator circuit and demonstrate the integration process.  
 ii) When the input is sinusoidal, demonstrate how the integrator performs as a filter. [2.5 Marks]
- c) i) Reproduce the circuit for a square wave oscillator based on a single operational amplifier.  
 ii) Name the circuit in part i).  
 iii) Explain the square wave generation process for the circuit in part i). [3.5 Marks]

- Q5 a) i) State three differences between Field Effect Transistors (FETs) and Bipolar Junction Transistors (BJTs).
- ii) Sketch the structure of a N-channel JFET indicating the terminals and show how it is biased for normal operation.
- iii) The self-bias circuit of a N- channel JFET shown in Figure Q5 a) has  $I_{DSS} = 12 \text{ mA}$  and  $V_P = -4.5 \text{ V}$ . Determine the Q point values of  $I_D$  and  $V_{DS}$  and show that the Q point is in the pinch-off region.

- b) i) Show that the trans-conductance ( $g_m$ ) for a JFET is given by

[4 Marks]

$$g_m = \frac{2I_{DSS}}{|V_P|} \sqrt{\frac{I_D}{I_{DSS}}} \quad \text{Seimens}$$

Hint:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

- ii) The JFET in the common source amplifier configuration shown in Figure Q5 b) has  $g_m = 4.2 \times 10^{-3} \text{ S}$  and  $r_d = 98 \text{ k}\Omega$ . Sketch the small signal ac equivalent circuit and calculate the voltage gain.
- c) i) State the two types of MOSFETs.
- ii) Draw the N-channel depletion type MOSFET characteristic curves and indicate all the regions of operation.
- iii) Sketch the voltage divider biasing circuit for an enhancement type N-channel MOSFET.

[4 Marks]

[2 Marks]

 


Figure Q5 a)

 


Figure Q5b)