



# UNIVERSITY OF RUHUNA

## Faculty of Engineering

End-Semester 2 Examination in Engineering: July 2022

Module Number: EE2202 Module Name: Introduction to Electronic Engineering

[Three Hours]

[Answer all questions, each question carries 10 marks]

- Q1 a) i) Briefly explain the concept of diffusion and drift of charge carriers in semiconductors.  
ii) Briefly explain how the PN junction behaves under the equilibrium state.

[3.0 Marks]

b) Figure Q1.1 shows a Si diode circuit used to add a dc level to a signal with an average value of zero.  $v_s$  is a square wave alternate between 10 V and -10 V. The period of the square wave is  $T$ .

- i) Plot the output ( $v_L$ ) over time ( $t$ ) considering the constant voltage model for the diode.  
ii) Find the average value of the output signal.

 


Figure Q1.1

[4.0 Marks]

- c) Figure Q1.2 shows the function ReLU (Rectified Linear Unit), which is used as an activation function in artificial neural networks. Propose a diode circuit to perform the ReLU function to a given input voltage, assuming that the diode is ideal.

 


Figure Q1.2

[3.0 Marks]

- Q2 a) i) State the three main regions of a BJT transistor and sort them based on doping levels.
- ii) State the rule for biasing along with the bias circuit with no external resistors and current equation for an *NPN* Si transistor in Common-Base configuration.
- iii) Sketch the output characteristics for a *NPN* Si transistor in common based configuration and saturation, active and cut-off regions.

[6.0 Marks]

b) Figure Q2 shows biased circuit with resistors for a *NPN* Si transistor in common based configuration.

- i) Derive an expression for the load line.
- ii) Find  $R_C$  and  $R_E$  of the circuit when  $V_{CB} = 4\text{ V}$ ,  $I_C = 3\text{ mA}$ ,  $V_{BE} = 0.7\text{ V}$ ,  $V_{CC} = -V_{EE} = 10\text{ V}$  and  $\beta = 120$ .

 


Figure Q2

[4.0 Marks]

Q3 a) Figure Q3.1 shows the schematic diagram of a transistor amplifier with the source and load.

- i) Derive an expression for the overall voltage gain ( $v_L/v_S$ ), where the voltage gain of the amplifier is  $A_v$ .
- ii) Based on the derived expression in part i), identify suitable input resistance (high or low) for a voltage amplifier.

 


Figure Q3.1

[3.0 Marks]

- b) Figure Q3.2 shows a CE amplifier in its simplest configuration.
- Briefly explain the role of  $C_{B1}$  and  $C_{B2}$  capacitors in the amplifier circuit.
  - Find the  $R_1$  and  $R_C$  to fix the Q-point at  $I_{CQ} = 30 \text{ mA}$  and  $V_{CEQ} = 10 \text{ V}$  ( $V_{CC} = 20 \text{ V}$ ,  $\beta = 50$ ).

 


Figure Q3.2

[4.0 Marks]

- c) Sketch the internal structure of an N-type Enhancement MOSFET, name the terminals and briefly explain the mechanism behind the formation of the N-channel in a biased E-MOSFET.

[3.0 Marks]

- Q4 a) Obtain the 1's and 2's complements of the following binary numbers.
- 11011010
  - 10000101

[3.0 Marks]

- b) Convert the following expressions to Product-of-Sums (PoS) form.
- $Z = A + \bar{B}CD$
  - $W = \bar{C}D + \bar{C}\bar{E} + \bar{G}H$

[3.0 Marks]

- c) Reconstruct the logic circuit shown in Figure Q4 using only NOR gates.

 


Figure Q4

[4.0 Marks]

Q5 a) Briefly explain the difference between combinational and sequential logic circuits using illustrations.

[2.0 Marks]

b) Simplify the following Boolean function  $F$ , together with don't care terms in  $d$ , using a four-variable Karnaugh map.

$$F(A, B, C, D) = \sum(2, 4, 6, 10, 12)$$

$$d(A, B, C, D) = \sum(0, 8, 9, 13)$$

[4.0 Marks]

c) Obtain the characteristic table for the clocked SR Flip-Flop shown in Figure Q5.

 


Figure Q5

[4.0 Marks]