



## University of Ruhuna- Faculty of Technology

Bachelor of Engineering Technology Honours Degree

Level I (Semester II) Examination, Nov.-Dec. 2025

Academic Year 2023/2024

Course Unit: TMS1222/ENT1242 Electromagnetics/E&M


Duration: 2 hours

### Instructions and details:

- Answer **All parts of Five (05)** questions.
- This question paper is composed of 4 pages.
- The paper carries a total of 100 marks, and each question carries 20 marks.
- Calculators are allowed for calculations.
- When relevant, answers should be expressed in terms of the given (relevant) variables and simplified.
- All symbols have their usual meanings.
- The solution of the differential equation  $\frac{dy}{dt} + by = 0$  can be written as  $y = ae^{-bt}$ , where  $a$  and  $b$  are constants.
- $k = \frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ Nm}^2/\text{C}^2$ .
- $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$ .
- $\mu_0 = 4\pi \times 10^{-7} \text{ T.m/A}$ .

1.

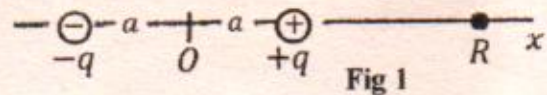- (i) In Figure 1, an electric dipole is located along the  $x$ -axis and it is centered at the origin  $O$ . It is made of two charges of equal magnitude  $q$  and opposite signs that are separated by a distance  $2a$ . Let  $k$  denote the Coulomb's constant.




- (a) Find the electrostatic force (magnitude) between the two charges of the dipole. (2 marks)  
 (b) Find the electric potential ( $V$ ) at point  $R(x, 0)$  on the  $x$ -axis as shown in the Figure. (5 marks)  
 (c) If the point  $R$  is located far away (such that  $x \gg a$ ) then, find the approximate potential at point  $R$ . (1 mark)
- (ii) A charged air-filled parallel-plate capacitor is made of plates of area  $A$  and plate separation  $d$ .

(a) When the surface charge density of each plate is  $\sigma$  (i.e., magnitude), the potential difference between the plates is given by  $|\Delta V| = \sigma d / \epsilon_0$ . Thus, find the capacitance of the capacitor in terms of  $\epsilon_0$ ,  $A$  and  $d$ . (3 marks) [\*Hint: Consider the definition of capacitance using charge  $Q$ .]

If  $A = 50 \text{ cm}^2$ ,  $d = 0.50 \text{ mm}$  and  $|\Delta V| = 500 \text{ V}$  then,

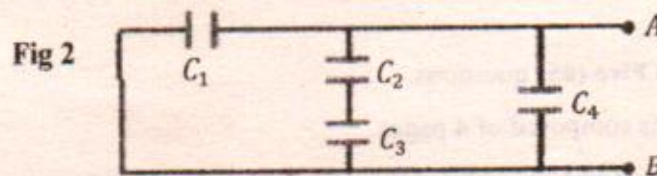- (b) Calculate the capacitance of the capacitor. (2 marks)  
 (c) Calculate the electric field (magnitude) between the plates of the capacitor. (2 marks)
- (iii) In a capacitor network four capacitors of capacitance each of  $10.0 \mu\text{F}$  are connected as shown in Figure 2.




A potential difference of  $10.0 \text{ V}$  is applied between the points  $A$  and  $B$ . Then,

- (a) Calculate the equivalent capacitance ( $C_{eq}$ ), between the points  $A$  and  $B$ . (3 marks)  
 (b) Calculate the total electrical energy stored in the capacitor network. (2 marks)

2.

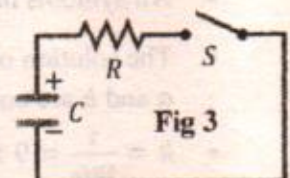- (i) The initial charge of the capacitor  $C$  of the  $RC$  circuit shown in Figure 3 is  $Q_0$ . The switch  $S$  is switched ON at time  $t = 0$ , and the capacitor discharges through the resistor.




- (a) Find an expression for the charge  $q$  of the capacitor at time  $t$ . (7 marks)

[\*Hints: Current  $i = -\frac{dq}{dt}$ . See the instructions given for the solution of differential equations.]

- (b) Find the current ( $i$ ) flowing through the circuit at time  $t$ . (4 marks)

- (ii) Figure 4 shows a straight conducting electrical wire segment of length  $l$ .

- (a) When  $\Delta V$  is the potential difference between the two end-points of the wire segment then, show that the electric field inside it can be written as  $E = \frac{|\Delta V|}{l}$ . (4 marks) [i.e., magnitude. \*Hint: Integration along  $x$ -axis.]

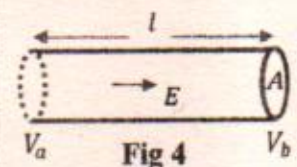

- (b) If the resistivity of the ohmic wire material is  $\rho$  and the circular cross-sectional area of the wire is  $A$  then, find the resistance ( $R$ ) of the wire segment in terms of  $\rho$ ,  $l$ , and  $A$ . (5 marks) [\*Hints: part-(a). Consider the current density  $J$ .]

3. In Figure 5, the resistances of the resistors are  $R_1 = 50.0 \Omega$ ,  $R_2 = R_5 = 25.0 \Omega$ , and  $R_3 = R_4 = 100 \Omega$  and the (ideal) batteries have emfs,  $\epsilon_1 = 6.00 \text{ V}$  and  $\epsilon_2 = 12.0 \text{ V}$ .

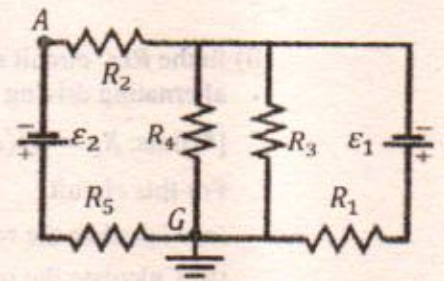


Fig 5

- Calculate the currents flowing in each resistor  $R_1$ ,  $R_2$ , and  $R_3$ . (12 marks) [\*Hints: You may want to simplify and redraw the circuit first.]
- Is the battery  $\epsilon_2$  is being charged or discharged? Briefly explain why. (2 marks)
- Calculate the power transfer in battery  $\epsilon_2$ . (2 marks)
- Calculate the combined power dissipated by both resistors  $R_3$  and  $R_4$ . (2 marks)
- If the point  $G$  of the circuit is grounded then, calculate the electric potential at point  $A$ . (2 marks)

4.

- (i) Figure 6 shows the cross-section of a long ideal solenoid coil (i.e., inductor) that carries a current  $i$  and has  $n$  turns per unit length.

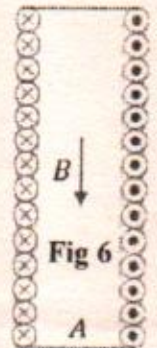


Fig 6

- Using Ampere's law, show that the uniform magnetic field generated inside the solenoid coil can be written as  $B = \mu_0 i n$ . (6 marks)
  - If the solenoid coil has a circular cross-sectional area  $A$  and a length  $l$  then, find the inductance ( $L$ ) of it. (4 marks)
  - A straight wire carrying a current  $i$  and of length  $L_0$  is placed at the midpoint of the solenoid coil perpendicular to its central axis. Find the magnetic force ( $F$ ) acting on the wire. (3 marks) [i.e., the magnitude]
- (ii) A wire of resistance  $1.0 \text{ m}\Omega$  forms a circular loop of diameter  $5.0 \text{ cm}$ . A uniform magnetic field  $\vec{B}$  is perpendicular to the plane of the wire loop. To induce a  $5.0 \text{ A}$  current in the loop, find the required rate of change of the magnitude of  $\vec{B}$ . (7 marks) [i.e., time rate. \*Hint: Faraday's law.]

5.

- (i) In the circuit shown in Figure 7, initially the switch  $S$  is in its ON position, and thus the inductors with inductances  $L_1$  and  $L_2$  are charged. Next, the switch  $S$  is switched OFF at time  $t = 0$  and just then the current flowing in the circuit is  $i_0$ . As the inductors discharge through the resistor with resistance  $R$ , find the current ( $i$ ) flowing in the circuit at time  $t$ . (7 marks) [\*Hints: first, you may want to replace both inductors with one. Self-induction  $\epsilon_L$ . See the instructions given for the solution of differential equations.]

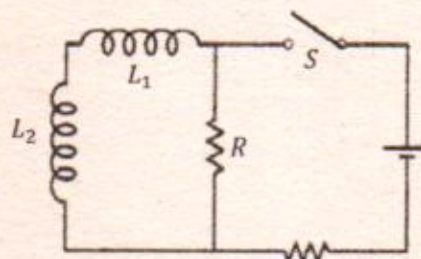



Fig 7

(ii) In the  $RLC$  circuit shown in Figure 8.  $R = 200 \Omega$ ,  $C = 100 \mu\text{F}$ ,  $L = 200 \text{ mH}$ , the amplitude of the alternating driving emf  $\mathcal{E}$  is  $\mathcal{E}_m = 40.0 \text{ V}$ , with a AC frequency of  $f_d = 60.0 \text{ Hz}$ .

[\*Hints:  $X_C = 1/(\omega_d C)$ ,  $X_L = \omega_d L$ ]

For this circuit.

- Calculate the reactance of the inductor  $L$ . (2 marks)
- Calculate the reactance of the capacitor  $C$ . (2 marks)
- Calculate the impedance ( $Z$ ) of the circuit. (2 marks)
- Calculate the power factor (PF) of the circuit. (1 mark)
- Calculate the root mean square (RMS) current flowing in the circuit. (2 marks)
- Calculate the combined RMS voltage across the  $R$  and  $C$  together. (2 marks)
- Calculate the average power that is dissipated by the circuit. (2 marks)

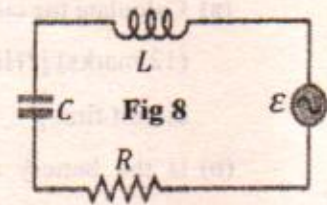

@@@@@@@@@@@@@@@@