



UNIVERSITY OF RUHUNA

Faculty of Engineering

End-Semester 1 Examination in Engineering: March 2026

Module Number: EE1301

Module Name: Fundamentals of Electricity (C-23)

[Three Hours]

[Answer all questions, each question carries 12.5 marks]

Q1 a) States the **Thevenin's theorem** with regard to circuit analysis.

[1.0 Mark]

b) i) By selecting the appropriate nodes, formulate **only** the necessary simultaneous equations to determine all node voltages of the DC circuit shown in Figure Q1(b)-1 using **Nodal Analysis**.

Assume that V_k ($1 \leq k \leq 10$; $k \in \mathbb{Z}$) represents the electric potential at the point k as indicated in Figure Q1(b)-1.

ii) Formulate **only** the necessary simultaneous equations to find all the mesh currents of DC circuit given in Figure Q1(b)-2 using **Mesh Analysis**.

Assume that I_k ($1 \leq k \leq 4$; $k \in \mathbb{Z}$) denotes the mesh current of the mesh k as indicated in Figure Q1(b)-2.

[6.5 Marks]

c) Use the **superposition theorem** to find the current (I_0) through the resistor of 2Ω in the DC circuit given in Figure Q1(c). Only **mesh analysis** must be used for all the circuit analysis in this part.

[5.0 Marks]

Q2 a) A single-phase AC source supplies a load as illustrated in Figure Q2(a). The source voltage, load voltage and load current are expressed in (Q2.1), (Q2.2) and (Q2.3), respectively.

$$e_a(t) = E_{am} \sin(\omega t + \delta) - (Q2.1)$$

$$v_L(t) = V_{Lm} \sin(\omega t) - (Q2.2)$$

$$i_L(t) = I_{Lm} \sin(\omega t - \theta) - (Q2.3)$$

i) Is the load inductive or capacitive? Justify your answer.

ii) Find expressions for the phasors of source voltage (E_a), load voltage (V_L) and load current (I_L).

iii) Determine the following parameters of $e_a(t)$.

I) Amplitude

IV) Frequency

II) RMS value

V) Phase angle

III) Average value

iv) Find an expression for the source voltage (E_a) in terms of V_L and I_L .

- v) Draw the phasor diagram of the electric circuit considering **all phasors**.
- vi) Considering the phasor diagram obtained in Part a)(v), show that the amplitude of $e_a(t)$ (E_a) can be expressed in (Q2.4).

$$E_a^2 = (V_L + I_L X_S \sin \theta)^2 + (I_L X_S \cos \theta)^2 \quad \text{--- (Q2.4)}$$

[4.0 Marks]

- b) A single-phase AC source supplies a load as illustrated in Figure Q2(b). The RMS voltage of the 50 Hz AC source is 120 V. The load impedance is $30 \angle 36^\circ \Omega$.
 - i) Find the impedances connected across terminals **a** and **b** (Z_{ab}).
 - ii) Calculate the source current (I_s).
 - iii) Calculate the voltage across the terminals **a** and **b** (V_{ab}).
 - iv) Find the load voltage and the load current.
 - v) Draw the phasor diagram of the electric circuit considering **all phasors**.

[4.5 Marks]

- c) A 480 V, 50 Hz single-phase AC source supplies a variable load as illustrated in Figure Q2(a). It is found that the amplitude of source voltage (E_a) is directly proportional to the frequency. The reactance of the circuit (X_s) is 3.5Ω at the nominal frequency. At a certain operating point, the load draws a current of 25 A and the load current lags the load voltage by 36° .
 - i) Calculate the load voltage (V_L).
 - ii) Calculate the load impedance.
 - iii) If the system frequency is increased to 60 Hz while keeping the same load impedance, calculate the new source voltage (E_a), load voltage (V_L) and load current (I_L).

[4.0 Marks]

- Q3 a) A single-phase f Hz AC source feeds a load. The phasors of load voltage, load current and source voltage are $V_L \angle 0^\circ$, $I_L \angle -\theta^\circ$ and $E_a \angle \delta^\circ$, respectively.
- i) Write an expression for the apparent load power (complex power) in terms of voltage and current phasors of the load.
 - ii) Hence, obtain expressions for apparent power, active power, and reactive power of the load.
 - iii) Draw the power triangle of the load clearly indicating apparent power, active power, and reactive power.
 - iv) Show that a capacitive load conventionally injects reactive power.
 - v) A capacitor bank is connected across the source to improve the input power factor. The improved power factor angle is α . Show that the required parallel capacitance (C_p) can be expressed in (Q3.1).

$$C_p = \frac{V_L I_L \cos \theta (\tan \theta - \tan \alpha)}{2\pi f E_a^2} \quad \text{--- (Q3.1)}$$

[4.5 Marks]

- b) A single-phase 50 Hz AC source supplies a 10 kVA load at 0.8 power factor lagging under the rated condition as illustrated in Figure Q3(b). The load voltage is 480 V.
- Calculate the load current (I_L).
 - Calculate the source voltage, source current and input power factor.
 - Find the apparent, real and reactive power supplied by the source.
 - Calculate the required parallel capacitance to improve the input power factor to 0.9 lagging.

[4.0 Marks]

- c) Consider the same circuit given in Figure Q3(b). At another operating point, the variable load mentioned in Section b) draws only 75% of the rated active power, while the **magnitudes of both the load and source voltages remain unchanged**.

- If the phasors of load voltage, load current and source voltage are $V_L \angle 0^\circ$, $I_L \angle -\theta^\circ$ and $V_S \angle \alpha^\circ$, respectively, draw the phasor diagram of the electrical system including only V_S , V_L and I_L phasors.

Hint : Use the expression of V_S in terms of V_L and I_L .

- Considering the phasor diagram drawn in Part c) (i), show that the active power drawn by the load (P_L) can be expressed in (Q3.2).

$$P_L = \frac{V_L V_S \sin \alpha}{X_s} \quad \text{--- (Q3.2)}$$

- Calculate the new phase angle of the source.
- Calculate the new load current and load power factor.

[4.0 Marks]

- Q4 a) Consider a three-phase positive (abc) sequence balanced delta-connected (Δ) load. If the instantaneous phase current across the terminal **a** and **b** is given by,

$$i_{ab}(t) = \sqrt{2} I_p \sin \omega t.$$

- Write expressions for all three instantaneous phase currents.
- Show that the phasor of line a current is $I_a = \sqrt{3} I_p \angle -30^\circ$.
- Derive the expressions for three-phase active power, reactive power, and apparent power using both phase parameters and line parameters separately. Use suffix ϕ and I to denote phase and line quantities, respectively.

[4.0 Marks]

- b) A three-phase balanced load is supplied by a positive (ABC) sequence balanced three-phase supply as illustrated in Figure Q4(b). The per-phase load impedance consists of a resistor and an inductor connected in parallel. The resistance of resistor and the reactance of inductor are 9 Ω and 8 Ω , respectively. The voltage across terminals A and B is 420 V.

- Calculate the per-phase equivalent load impedance.
- Calculate the line current of line A (I_A).
- Sketch the three-phase phasor diagram showing all the line-to-line voltages, line currents and phase currents.
- What is the power factor of the load.

- v) Calculate the total active power, reactive power and apparent power drawn by the three-phase load.

[5.5 Marks]

- c) A three-phase 480 V, 50 Hz, positive (abc) sequence, star connected balanced voltage source supplies a 8 kVA three-phase delta connected balanced load at 0.7 power factor lagging under the rated conditions.

- i) Calculate the phase current and line current of the load.
- ii) Calculate the required per phase parallel capacitance connected at the source side to improve the power factor to 0.9 lagging.

[3.0 Marks]

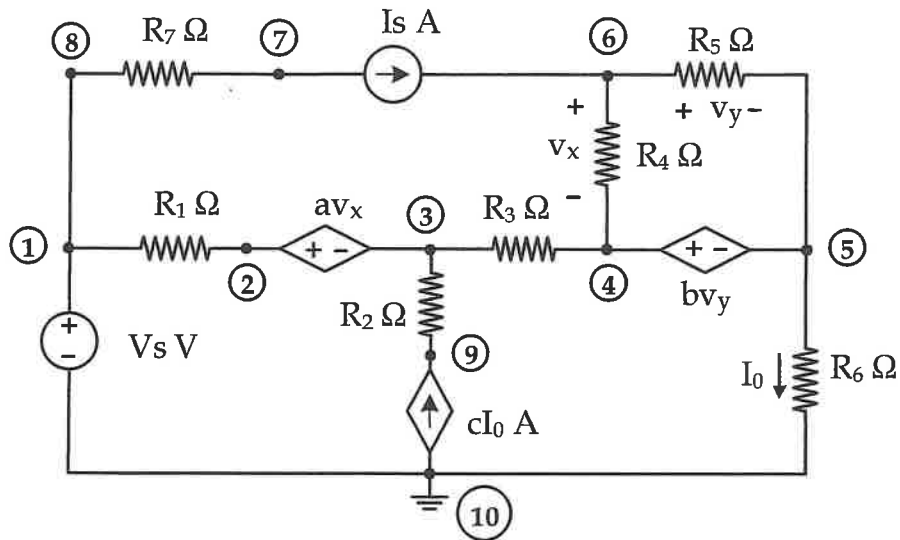


Figure Q1(b)-1

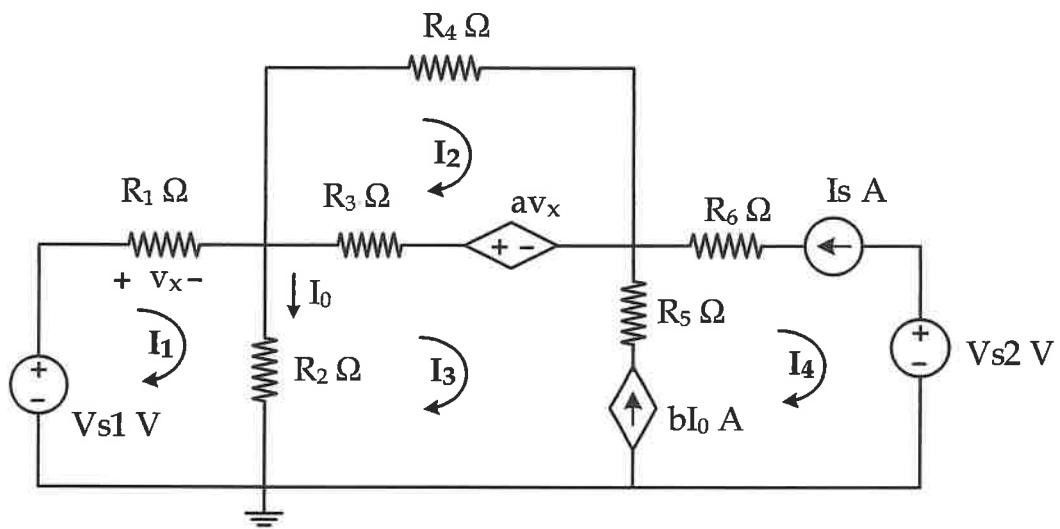


Figure Q1(b)-2

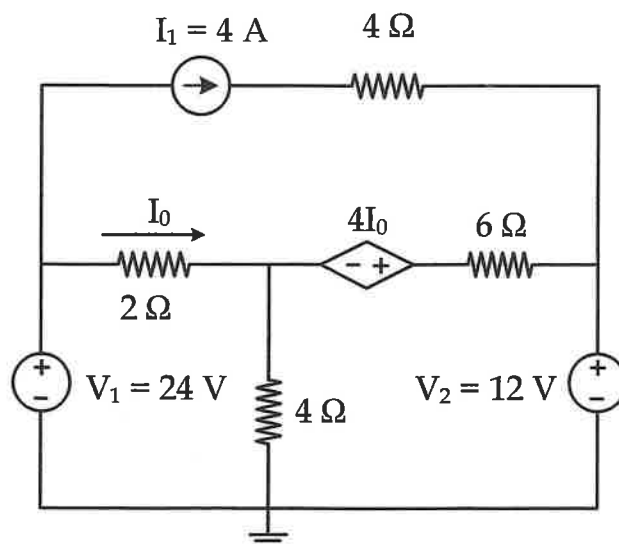


Figure Q1(c)

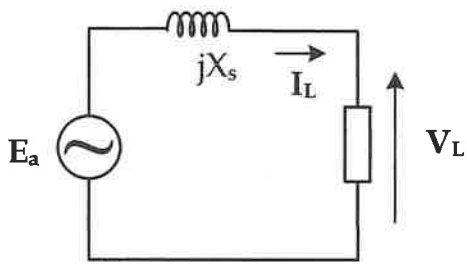


Figure Q2(a)

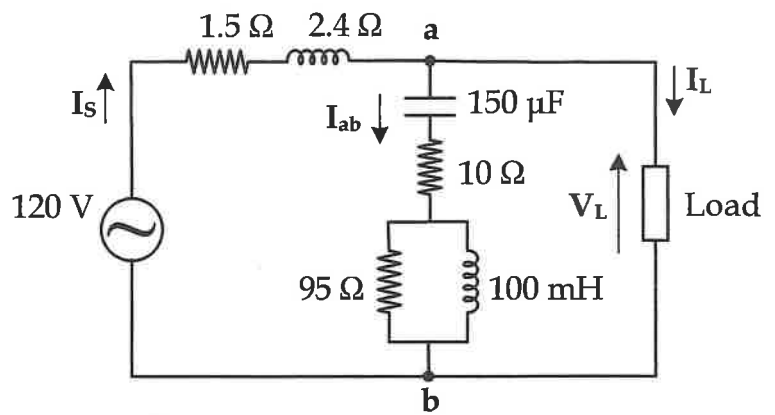


Figure Q2(b)

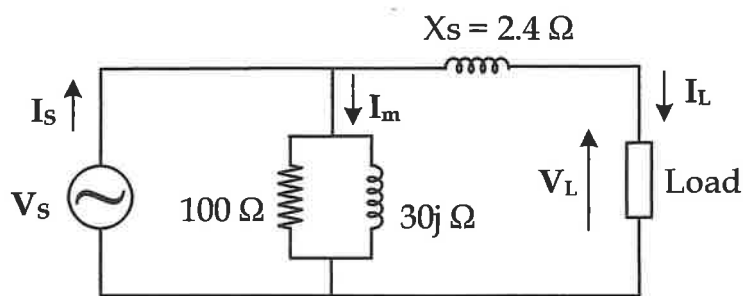


Figure Q3(b)

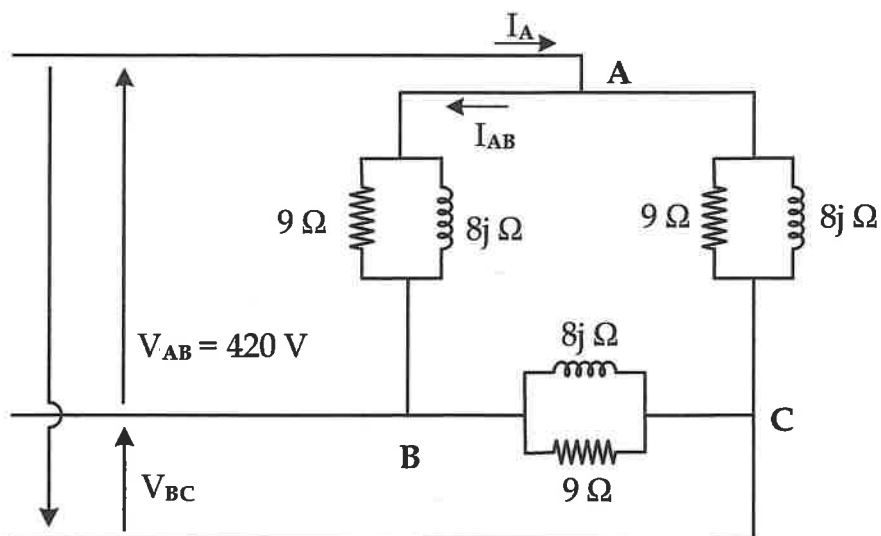


Figure Q4(b)