



UNIVERSITY OF RUHUNA

Faculty of Engineering

End-Semester 1 Examination in Engineering: March 2026

Module Number: EE1302 Module Name: Introduction to Electrical Engineering (C-18)

[Three Hours]

[Answer all questions, each question carries 12.5 marks]

Q1 a) States the **Thevenin's theorem** with regard to circuit analysis.

[1.0 Mark]

b) i) By selecting the appropriate nodes, formulate **only** the necessary simultaneous equations to determine all node voltages of the DC circuit shown in Figure Q1(b)-1 using **Nodal Analysis**.

Assume that V_k ($1 \leq k \leq 10$; $k \in \mathbb{Z}$) represents the electric potential at the point k as indicated in Figure Q1(b)-1.

ii) Formulate **only** the necessary simultaneous equations to find all the mesh currents of DC circuit given in Figure Q1(b)-2 using **Mesh Analysis**.

Assume that I_k ($1 \leq k \leq 4$; $k \in \mathbb{Z}$) denotes the mesh current of the mesh k as indicated in Figure Q1(b)-2.

[6.5 Marks]

c) Use the **superposition theorem** to find the current (I_0) through the resistor of 2Ω in the DC circuit given in Figure Q1(c). Only **mesh analysis** must be used for all the circuit analysis in this part.

[5.0 Marks]

Q2 a) i) What are the main protective mechanisms used in domestic electrical installation? Write one protective device for each protective mechanism.

ii) What is the difference between neutral earthing and equipment earthing?

iii) What are the three basic earthing systems available? Using suitable sketches, briefly explain how they differ from each other.

iv) What are the main types of electric circuits employed in a domestic electrical installation?

v) Final electric circuits of a domestic installation are protected with Miniature Circuit Breakers (MCBs). Briefly explain the operation of an MCB during short circuit and overloading faults.

vi) Briefly explain the operation of a Residual Current Circuit Breaker (RCCB) in the event of leakage fault in the domestic installation.

[6.0 Marks]

b) The switch of the Resistor, Inductor and Capacitor (RLC) circuit shown in Figure Q2(b) is closed for a significant time and it opens at $t=0$.

- i) Derive the differential equation which governs the behavior of the voltage across the capacitor for $t \geq 0$.
- ii) Obtain the characteristic equation of the given DC circuit in Figure Q2(b).
- iii) If the DC circuit is critically damped, show that,

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}.$$

- iv) If $R_L = 5 \Omega$, $R = 6 \Omega$, $L = 1 \text{ H}$, $C = 1/9 \text{ F}$ and $V_S = 25 \text{ V}$, find the total response of the capacitor voltage $v(t)$ for $t > 0$.
- v) Find the inductor current $i(t)$ for $t > 0$.

[6.5 Marks]

Q3 a) A single-phase f Hz AC source feeds a load. The phasors of load voltage, load current and source voltage are $V_L \angle 0^\circ$, $I_L \angle -\theta^\circ$ and $E_a \angle \delta^\circ$, respectively.

- i) Write an expression for the apparent load power (complex power) in terms of voltage and current phasors of the load.
- ii) Hence, obtain expressions for apparent power, active power, and reactive power of the load.
- iii) Draw the power triangle of the load clearly indicating apparent power, active power, and reactive power.
- iv) Show that a capacitive load conventionally injects reactive power.
- v) A capacitor bank is connected across the source to improve the input power factor. The improved power factor angle is α . Show that the required parallel capacitance (C_p) can be expressed in (Q3.1).

$$C_p = \frac{V_L I_L \cos \theta (\tan \theta - \tan \alpha)}{2\pi f E_a^2} \quad - (Q3.1)$$

[4.5 Marks]

b) A single-phase 50 Hz AC source supplies a 10 kVA load at 0.8 power factor lagging under the rated condition as illustrated in Figure Q3(b). The load voltage is 480 V.

- i) Calculate the load current (I_L).
- ii) Calculate the source voltage, source current and input power factor.
- iii) Find the apparent, real and reactive power supplied by the source.
- iv) Calculate the required parallel capacitance to improve the input power factor to 0.9 lagging.

[4.0 Marks]

c) Consider the same circuit given in Figure Q3(b). At another operating point, the variable load mentioned in Section b) draws only 75% of the rated active power, while the **magnitudes of both the load and source voltages remain unchanged.**

- i) If the phasors of load voltage, load current and source voltage are $V_L \angle 0^\circ$, $I_L \angle -\theta^\circ$ and $V_S \angle \alpha^\circ$, respectively, draw the phasor diagram of the electrical system including only V_S , V_L and I_L phasors.

Hint : Use the expression of V_S in terms of V_L and I_L .

- ii) Considering the phasor diagram drawn in Part c) (i), show that the active power drawn by the load (P_L) can be expressed in (Q3.2).

$$P_L = \frac{V_L V_S \sin \alpha}{X_S} \quad \text{--- (Q3.2)}$$

- iii) Calculate the new phase angle of the source.
iv) Calculate the new load current and load power factor.

[4.0 Marks]

- Q4 a) Consider a three-phase positive (abc) sequence balanced delta-connected (Δ) load. If the instantaneous phase current across the terminal a and b is given by,

$$i_{ab}(t) = \sqrt{2} I_p \sin \omega t.$$

- i) Write expressions for all three instantaneous phase currents.
ii) Show that the phasor of line a current is $I_a = \sqrt{3} I_p \angle -30^\circ$.
iii) Derive the expressions for three-phase active power, reactive power, and apparent power using both phase parameters and line parameters separately. Use suffix ϕ and l to denote phase and line quantities, respectively.

[4.0 Marks]

- b) A three-phase balanced load is supplied by a positive (ABC) sequence balanced three-phase supply as illustrated in Figure Q4(b). The per-phase load impedance consists of a resistor and an inductor connected in parallel. The resistance of resistor and the reactance of inductor are 9Ω and 8Ω , respectively. The voltage across terminals A and B is 420 V.

- i) Calculate the per-phase equivalent load impedance.
ii) Calculate the line current of line A (I_A).
iii) Sketch the three-phase phasor diagram showing all the line-to-line voltages, line currents and phase currents.
iv) What is the power factor of the load.
v) Calculate the total active power, reactive power and apparent power drawn by the three-phase load.

[5.5 Marks]

- c) A three-phase 480 V, 50 Hz, positive (abc) sequence, star connected balanced voltage source supplies a 8 kVA three-phase delta connected balanced load at 0.7 power factor lagging under the rated conditions.

- i) Calculate the phase current and line current of the load.
ii) Calculate the required per phase parallel capacitance connected at the source side to improve the power factor to 0.9 lagging.

[3.0 Marks]

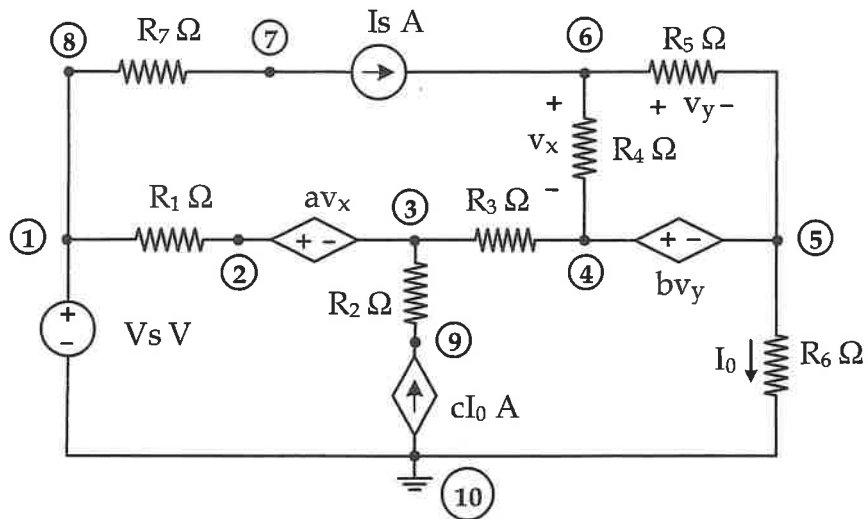


Figure Q1(b)-1

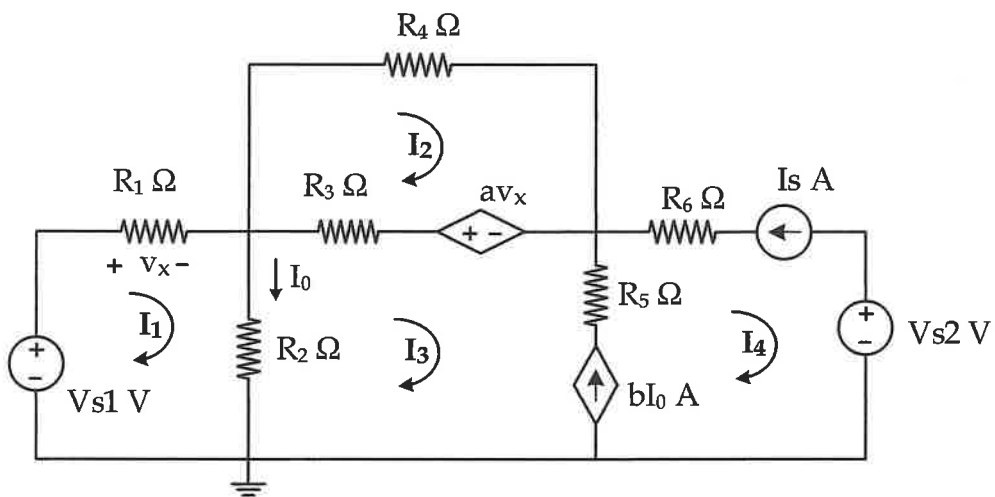


Figure Q1(b)-2

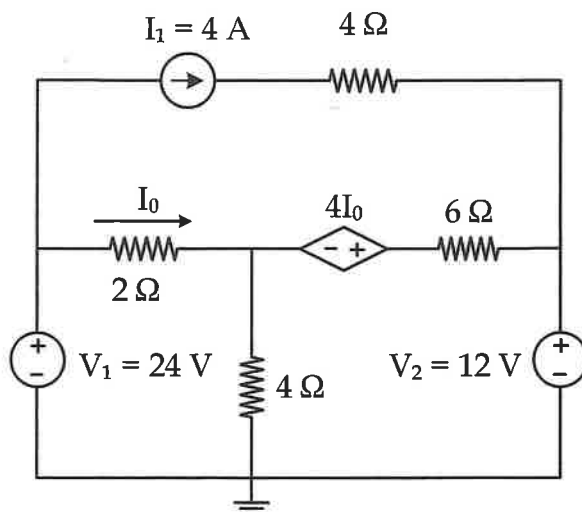


Figure Q1(c)

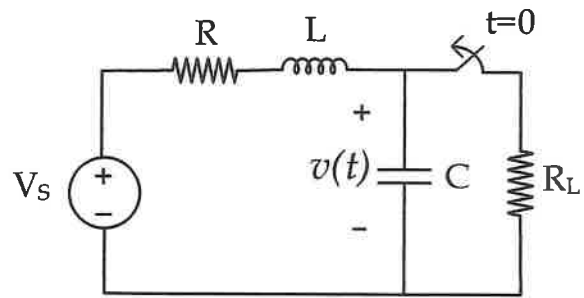


Figure Q2(b)

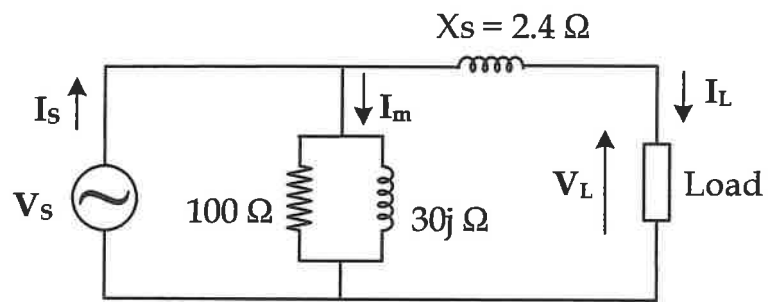


Figure Q3(b)

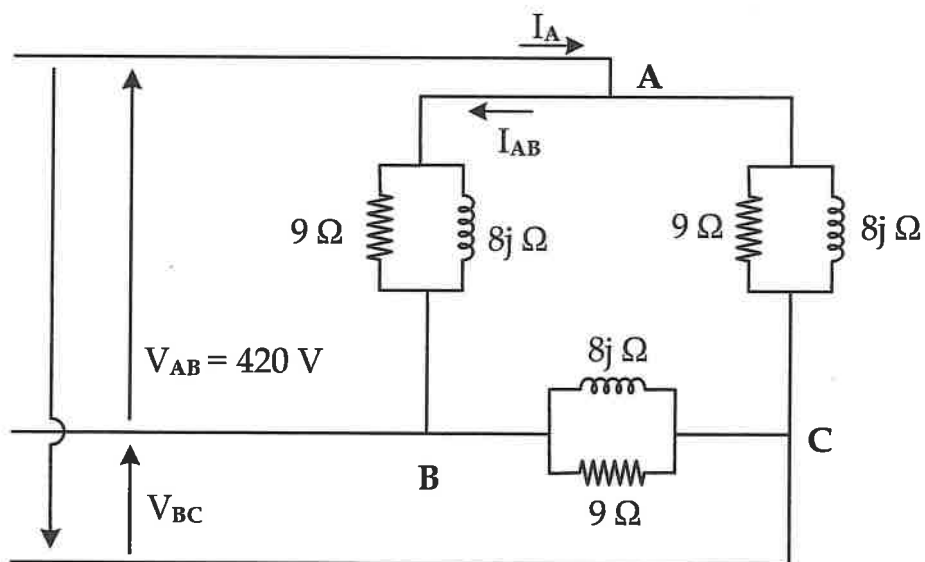


Figure Q4(b)

