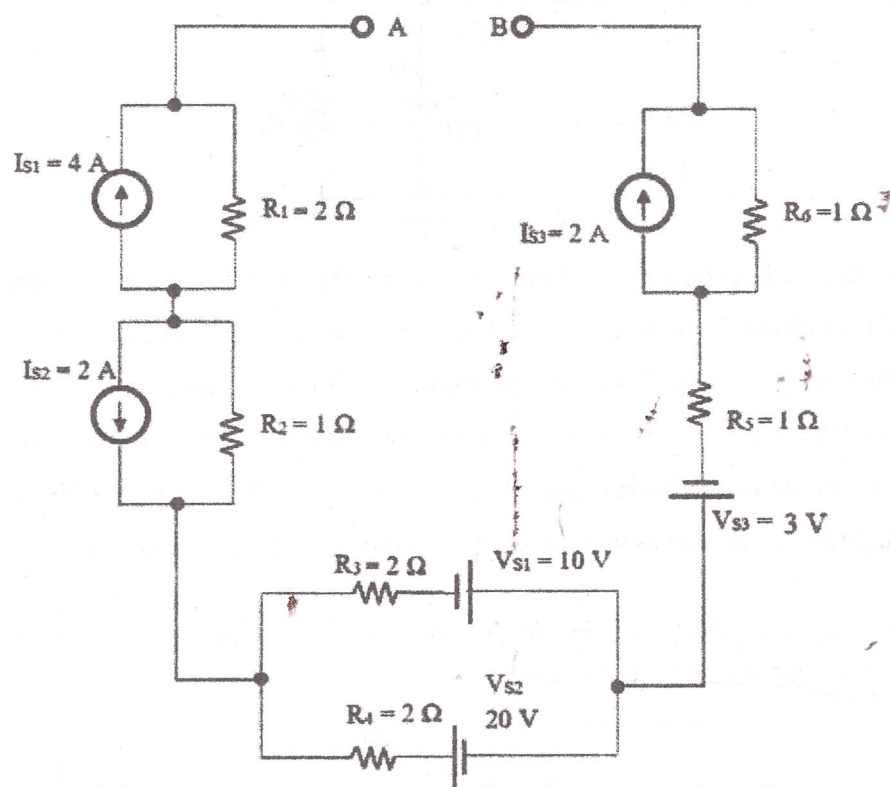


University of Ruhuna
Bachelor of Science (General) Degree Level II (Semester I) Examination
July - 2023

Subject: Physics
Course Unit: PHY 2112

PART B - 1 hour & 15 minutes
Answer FIVE questions only.
All symbols have their usual meaning.


1. Consider the circuit shown below.



- (a) Use source conversions to find the Thevenin's equivalent circuit across **A** and **B** terminals. [4 Marks]
- (b) If a load resistor (R_L) is connected across **A** and **B** terminals, derive expressions for voltage across and current through the load resistor in terms of V_{TH} , R_{TH} and R_L . [2 Marks]
- (c) Hence, find the maximum voltage across and maximum current through a load resistor. [2 Marks]
- (d) What would be the value of R_L to deliver the maximum power from the circuit to a load resistor and find the maximum power? [2 Marks]


2.

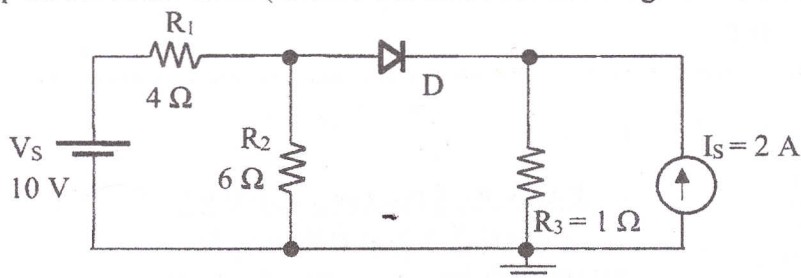- (a) Find the voltage across and current through the diode given in the following circuit using the constant voltage drop model of the diode (assume that diode cut-in voltage of the diode (V_{D0}) is 0.7 V)




[5 Marks]

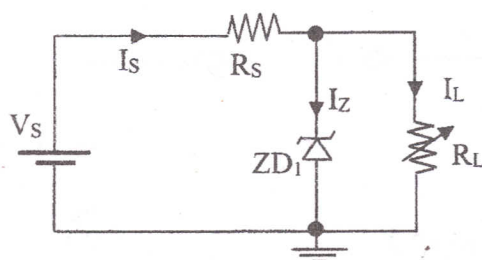- (b) Answer the following parts considering the circuit given below. Use the constant voltage drop model of a Zener diode.




- (a) If the Zener diode operates in the reverse active region, derive an expression for the current through the Zener diode (I_Z) in terms of V_S , R_S , I_L and V_{Z0} (Zener breakdown voltage). [3 Marks]
- (b) If the supply voltage (V_S) changes from 15 V to 25 V, estimate the sustainable maximum and minimum current for the load resistor that can be drawn without disrupting the voltage regulation process of the Zener diode (Take, if $R_S = 100 \Omega$, $V_{Z0} = 5$ V, minimum Zener current for the reverse breakdown is 1mA and maximum power dissipation of the Zener diode is 1 W). [2 Marks]

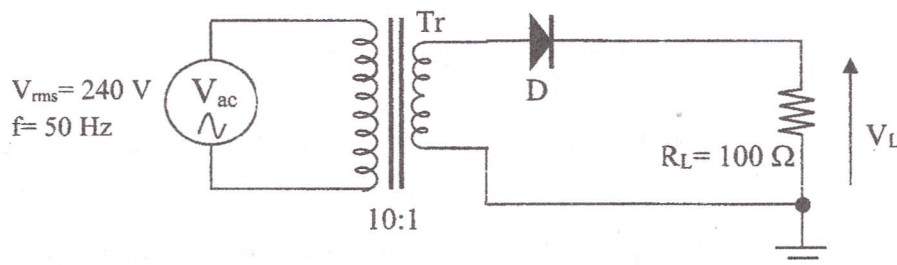3. Answer the following questions considering the rectifier circuit given below. Neglect the resistance of the secondary winding of the transformer.




- (a) Calculate the followings (consider the diode as ideal).
- i The peak value of the voltage across R_L , [2 Marks]
 - ii The rms value of the voltage across R_L , [1 Marks]
 - iii Value of the d.c. component of the voltage across R_L , [2 Marks]
 - iv rms value of the a.c. components of the voltage across R_L [2 Marks]
- (b) Sketch the wave pattern of the voltage across the load resistor (R_L) if the polarity of the diode is reversed. [3 Marks]

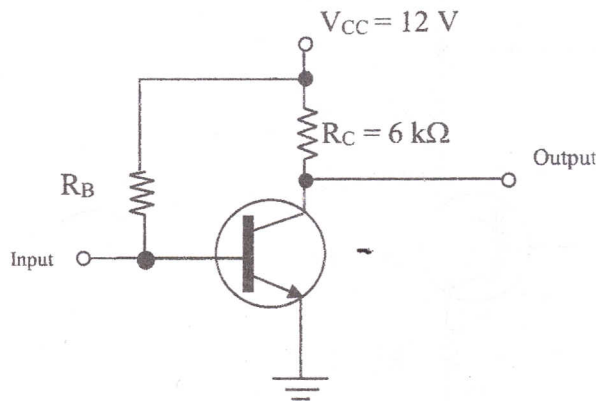4. Consider the following biasing circuit of a common emitter transistor amplifier circuit. ($\beta = 100$, $V_{CE(SAT)} = 0$ V, and V_{BE} is negligible for this transistor).



- What value should the V_{CE} (the voltage across collector to emitter) be held to obtain the distortion-free maximum output signal? [2 Marks]
- Calculate the appropriate value for R_B to maintain the value of V_{CE} that mentioned in part (a) above. [4 Marks]
- What will be the value of V_{CE} and I_C with the same R_B calculated above if R_C is replaced by a 5 kΩ resistor? [4 Marks]

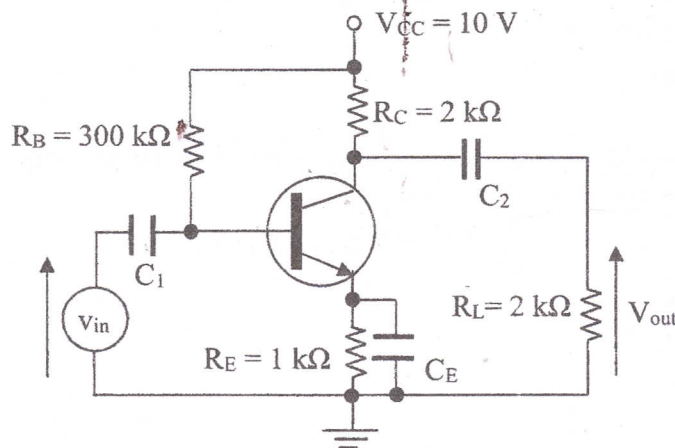
5. Consider the following amplifier circuit (take $\beta = 100$)



- What is the configuration of this transistor amplifier? [Marks 2]
- Calculate I_E of the above circuit. (Assuming V_{BE} is very small and $I_E \approx I_C$). [Marks 3]
- Draw the ac equivalent circuit for the above circuit. Hence, find the alternating current (ac) voltage gain. [Marks 5]

Take emitter intrinsic resistance, $r_e' = \frac{25 \text{ mV}}{I_E}$.

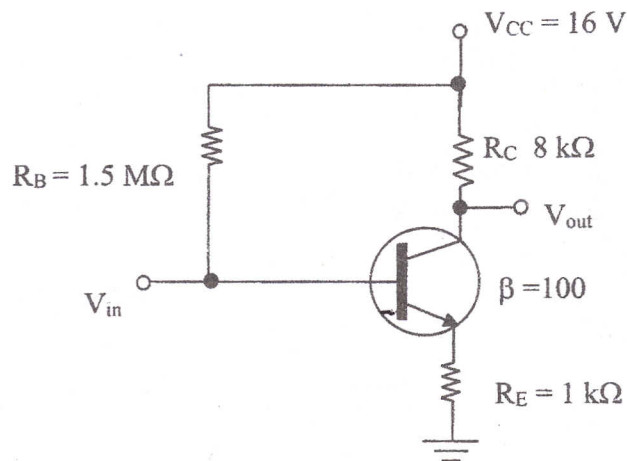6. Write down the expression of the closed-loop gain for a negative feedback amplifier by defining terms. [2 Marks]



- (a) Derive an expression for the closed-loop gain of the above negative feedback amplifier in terms of R_C , R_E and emitter intrinsic resistance (r_e) [3 Marks]
- (b) Using the above expressions, calculate the open-loop gain and feedback fraction of the amplifier. [Take $r_e' = \frac{25 \text{ mV}}{I_E}$, common emitter current gain of the transistor (β) is 100, and V_{BE} is negligible.] [3 Marks]
- (c) If the open-loop gain of the above feedback amplifier changes by 25 % due to a temperature variation, find the percentage change in closed-loop gain. [2 Marks]

7.

- (a) Prove the following identities using Boolean algebra. [3 Marks]
- $A \cdot (A + A \cdot B) + \bar{A} \cdot B = A + B$ [3 Marks]
 - $\overline{\bar{A} + A \cdot \bar{B}} = A \cdot B$
- (b) Simplify the following expression using a Karnaugh-Map (K-Map). [4 Marks]
- $$X = A \cdot B \cdot \bar{C} + B \cdot C \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot D$$
- @@@@@@@@@@@@